

Digital Logic Systems

Sequential Logic

Assist. Prof. Özge ÖZTİMUR KARADAĞ
ALKÜ

Last Week


- Completed Combinational Circuits
 - Decoder
 - Encoder
 - Multiplexer
- Able to design/analyze combinational circuits with any combination of logic gates, decoders, multiplexers.
- Can design decoders / multiplexers by combining decoders / multiplexers in various sizes.

Digital Logic Systems

- Digital Logic Design:
Combinational Circuits




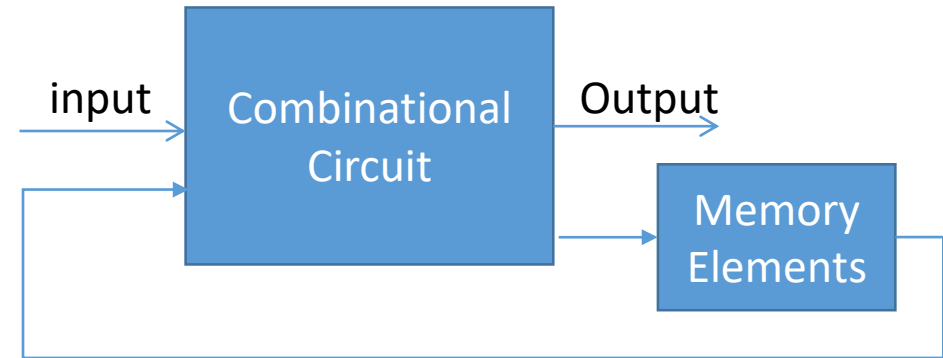- Digital Logic Systems:
Sequential Circuits



Synchronous Sequential Logic

Block Diagram of Sequential Circuit

 



- Memory Elements
 - Store binary data.
 - This data is referred as the current state of the flip-flop.
- Sequential Circuit
 - Determines the output using input and the current state.
 - Input and the current state determine the next state.

Sequential Circuit

- is defined by?
 - Time
 - input
 - output
 - state
- Types:
 - **Synchronous sequential Circuit:** A *synchronous* sequential circuit is a system whose behavior can be defined from the knowledge of its signals at discrete instants of time.
 - **Asynchronous sequential Circuit:** The behavior of an *asynchronous* sequential circuit depends upon the input signals at any instant of time *and* the order in which the inputs change.

Types of Sequential Circuits

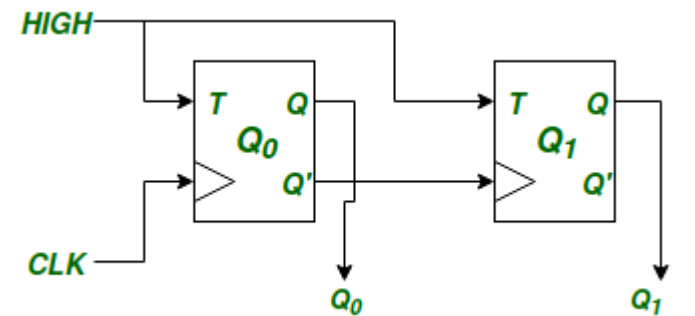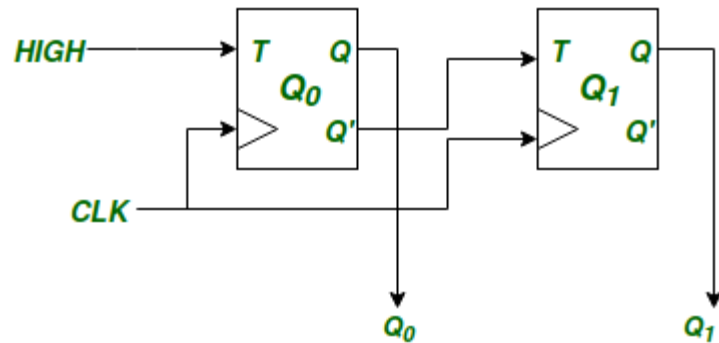- Synchronous Sequential Circuit
- Asynchronous Sequential Circuit




Synchronous Sequential Circuit

- Employs signals that affect the storage elements at only discrete instant of time.
- Synchronization is achieved by a timing device called a *clock* generator which provides a clock signal having the form of a periodic train of *clock pulses*.
- The clock pulses are distributed throughout the system in such a way that storage elements are affected only with the arrival of each pulse.
- The clock pulses determine *when* computational activity will occur
- Other signals (external inputs and otherwise) determine *what* changes will take place affecting the storage elements and the outputs

Memory Elements

- Flip-flop: A flip-flop is a binary storage device capable of storing one bit of information.
- Flip-flop has two outputs.
 - Bit which determines the state of the flip-flop.
 - Complement of the bit representing the state of the flip-flop.
- Depending on the number of bits represented by the sequential circuit, the number of flip-flops is determined.

Synchronous Sequential Circuit

 

(a) Block diagram




(b) Timing diagram of clock pulses

Flip-Flops

- A flip-flop can hold its state until an input signal is asserted to change its state.
- Types of Flip-flops vary:
 - By the number of input signals.
 - How the inputs effect the binary state of the flip-flop.

A Simple Flip-flop Circuit

x	y	x NOR y
0	0	1
0	1	0
1	0	0
1	1	0

 

(a) Logic diagram

S	R	Q	Q'
1	0	1	0
0	0		
0	1		
0	0		
1	1		

(after $S = 1, R = 0$)

(after $S = 0, R = 1$)

(forbidden)

(b) Function table


Q state of the flip-flop, Q' complement of Q.

Q=1, Q'=0 set

Q=0, Q'=1 reset

Flip-Flop with NAND Gates

x	y	x NAND y
0	0	1
0	1	1
1	0	1
1	1	0

 

(a) Logic diagram

S	R	Q	Q'
1	0	0	1
1	1	[Blue box]	
0	1		
1	1	[Blue box]	
0	0		

(after $S = 1, R = 0$)
(after $S = 0, R = 1$)
(forbidden)

(b) Function table


RS Flip-Flop

	00	01	11	10
0			X	1
1	1		X	1


$Q(t+1) = S + R'Q$
 $SR = 0$
Characteristic Equation

Q	S	R	Q(t+1)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Characteristic Table

 

(a) Logic diagram

 

(b) Function table


D Flip-Flop

Q	D	Q(t+1)
0	0	?
0	1	
1	0	
1	1	

Characteristic Table

	0	1
0		1
1		1

$Q(t+1)=D$
Characteristic Equation

 


(a) Logic diagram


?

(b) Function table

J-K Flip-Flop

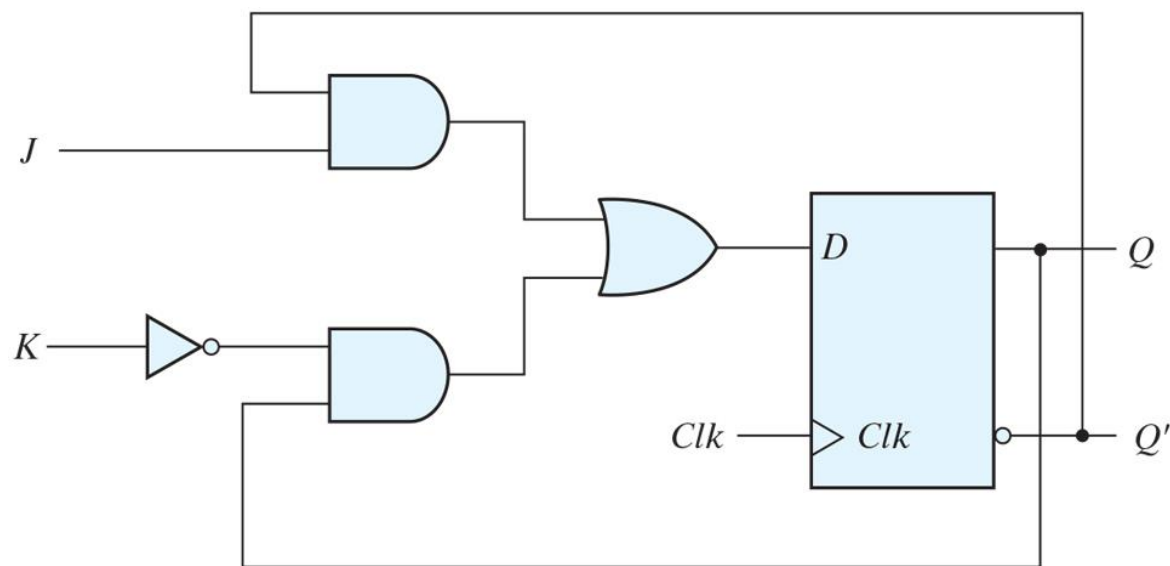

(a) Circuit diagram

 

(b) Graphic symbol

	00	01	11	10
0			1	1
1	1			1


$$Q(t+1) = JQ' + K'Q$$

Characteristic Equation


Q	J	K	Q(t+1)
0	0	0	?
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Characteristic Table


T Flip-Flop

 

(a) From JK flip-flop

 

(b) From D flip-flop

 

(c) Graphic symbol

Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0




Characteristic Table

	0	1
0		1
1	1	

$$Q(t+1) = TQ' + T'Q$$

Characteristic Equation

Graphical Symbols of Flip-Flops

   

Flip-Flop and Clock Signal

- If flip-flops respond to a **level of clock**, indetermined conditions may arise.
 - If the flip-flop outputs change while the output of the combinational circuit which are fed as input to flip flops then indetermined condition arises.
- Solution: Flip-flops respond to **clock transitions**..



(a) Response to positive level




(b) Positive-edge response



 
(c) Negative-edge response

Positive Edge Triggered D Flip-Flop


- For the third flip-flop
 - $S=0, R=1 \rightarrow Q=1$
 - $S=1, R=0 \rightarrow Q=0$
- 4 conditions:
 - $CP=0, D=0 \rightarrow$
 - $R=1, S=1 \rightarrow$ Forbidden
 - $CP=0, D=1 \rightarrow$
 - $R=1, S=1 \rightarrow$ Forbidden
 - $CP=1, D=0 \rightarrow$
 - $R=0, S=1 \rightarrow Q=0$
 - $CP=1, D=1 \rightarrow$
 - $R=1, S=0 \rightarrow Q=1$
- Summary: When the input CLK signal changes make a positive transition, value of D is transferred to Q.
- When CP is always 1 changes in D are not transferred to Q.



 Graphical Representation of Edge Triggered D Flip-Flops



(a) Positive-edge

 

(b) Negative-edge

Flip-Flop Characteristic Tables

<i>JK</i> Flip-Flop			
<i>J</i>	<i>K</i>	$Q(t + 1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

<i>D</i> Flip-Flop		
<i>D</i>	$Q(t + 1)$	
0	0	Reset
1	1	Set

<i>T</i> Flip-Flop		
<i>T</i>	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

- Questions?

References

- Morris Mano, Digital Design