

# COM 204 – Digital Logic Systems

Assist. Prof. Özge ÖZTİMUR KARADAĞ

- Assist. Prof. Özge ÖZTİMUR KARADAĞ
  - Email: [ozge.karadag@alanya.edu.tr](mailto:ozge.karadag@alanya.edu.tr)
- Asistant: Gürkan Çelik
  - Email: [gurkan.celik@alanya.edu.tr](mailto:gurkan.celik@alanya.edu.tr)

# Digital Logic Systems– COM 204

- Prerequisite: Digital Logic Design
- Book: Morris Mano, Digital Design, 4th edition
- **Evaluation:**
  - Midterm                      Quantity:1                      Percentage: 40%
  - Final                      :                      Quantity:1                      Percentage : 60%

# Weekly Plan

Week	
21 February	Introduction, Material Related to Combinational Circuit
28 February	Synchronous Sequential Logic: Analysis of Clocked Sequential Circuits
7 March	Synchronous Sequential Logic: State Reduction and Assignment, Flip-Flop Excitation Tables
14 March	Design of Counters, Problems
21 March	Registers, Shift Registers
28 March	Ripple Counters, Synchronous Counters
4 April	Timing, Problems
10-16 April	Midterm (tentative)
18 April	Random Access Memory (RAM), Memory Decoding, Error Detection and Correction
25 April	ADM (Algorithmic State Machine), Realization of the Control Circuit
2 May	ADM
9 May	ADM: Design with Multiplexers
16 May	ADM: PLA (Programmable Logic Array)
23 May	Asynchronous Sequential Logic: Analysis
30 May	Asynchronous Sequential Logic: Design Procedure

The plan is tentative. Possible changes will be announced during lectures.



- Lab will start in April. Follow the announcements.
- Questions??

# Digital Logic Design

- Binary System
- Boolean Algebra and Logic Gates
- Combinational Circuits
  - Binary adder-subtractor
  - Decoder
  - Encoder
  - Multiplexer
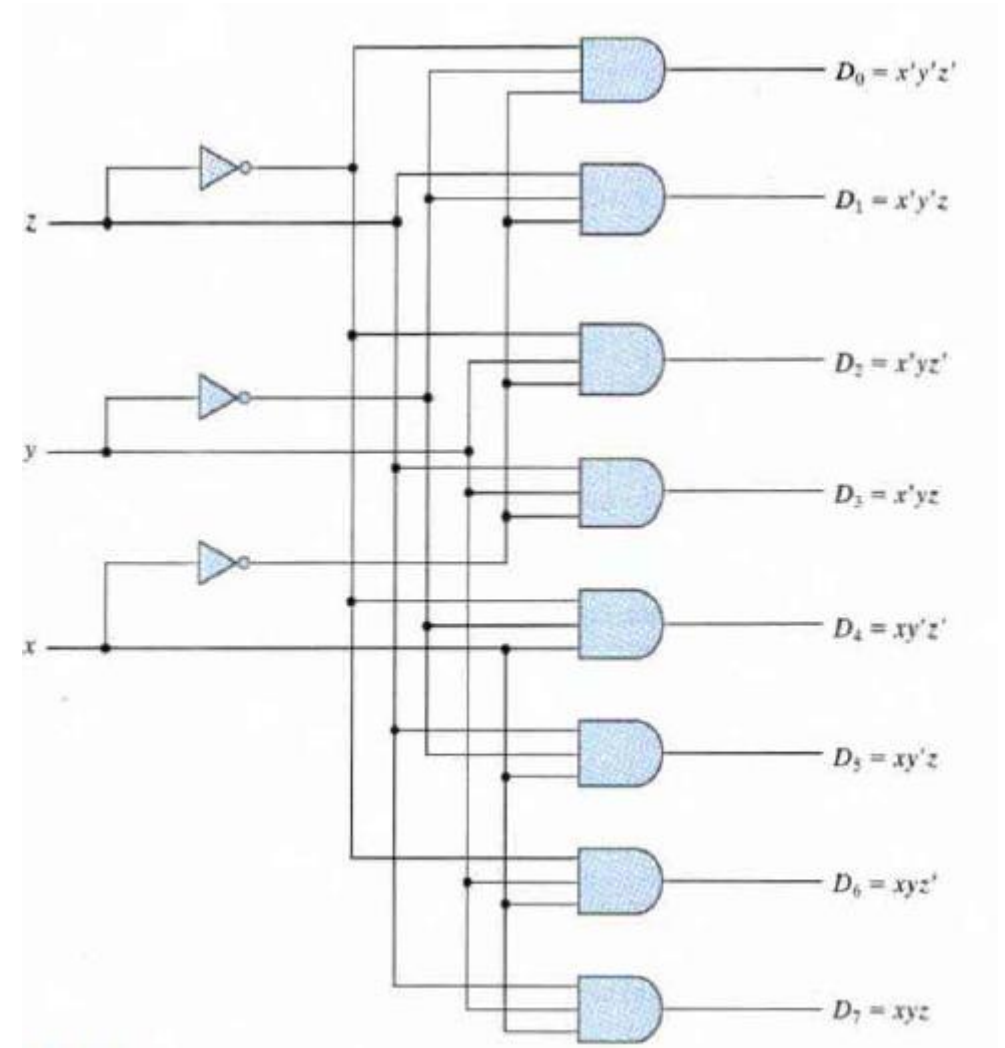 
# DECODERS

- A decoder is a combinational circuit that converts Binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines.
- $n$ -to- $m$  line decoders, where  $m \leq 2^n$
- Ex: three-to-eight line decoder



# DECODERS

- Three-to-eight line decoder (Binary-to-octal conversion)


Inputs			Outputs							
<i>x</i>	<i>y</i>	<i>z</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>	<i>D</i> <sub>4</sub>	<i>D</i> <sub>5</sub>	<i>D</i> <sub>6</sub>	<i>D</i> <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1



# DECODERS

- Ex: two-to-four line decoder with **enable** input
  - Circuit is disabled when  $E=1$

$E$	$A$	$B$	$D_0$	$D_1$	$D_2$	$D_3$
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

 


# DECODERS

- A decoder may operate with complemented or uncomplemented outputs.
- The enable input may be activated with a 0 or a 1 signal.
- Some decoders have two or more enable inputs that must satisfy a given logic condition in order to enable the circuit.

# DECODERS


- Demultiplexer: A circuit that receives information from a single line and directs it to one of  $2^n$  possible output lines. The selection of the specific output is controlled by the bit combination of  $n$  selection lines.
- A decoder with enable input can function as a demultiplexer.
  - In the figure, one-to-four line demultiplexer
    - E is the input
    - A and B are selection inputs
    - Ex: if selection  $AB=10$ , output  $D_2$  will be same as E.

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

 
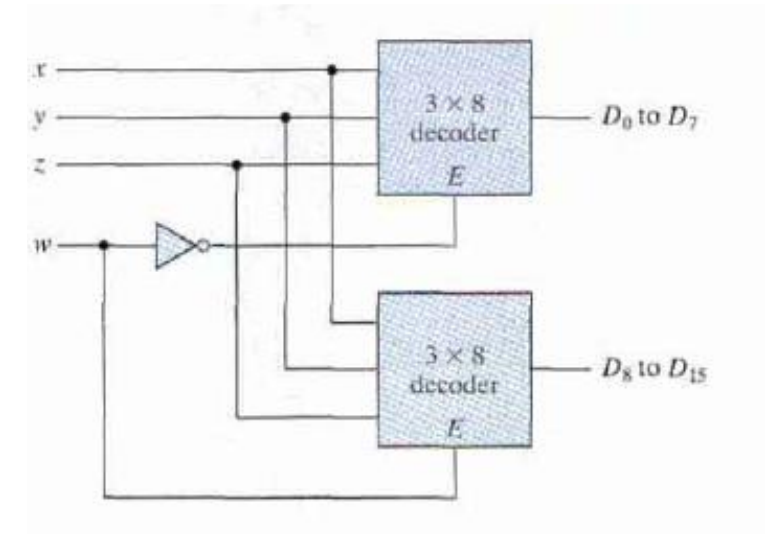
# DECODERS

- Decoders with enable inputs can be connected to form a larger decoder circuit.
- Ex: 3-to-8 line decoders with enable inputs connected to form a 4-to-16 line decoder.
  - $w=0$ : top decoder is enabled, the other is disabled  
bottom decoder outputs are all 0's.  
top eight outputs generate minterms 0000 to 0111
  - $w=1$ : top decoder is disabled, the other is enabled,  
the bottom decoder outputs generate minterms 1000 to 1111  
the outputs of top decoder are all 0's



# DECODERS

- Any Boolean Function can be represented in Sum of Products form.
- A decoder provides all minterms as its outputs.
- So any Boolean function with  $n$  inputs and  $m$  outputs can be implemented using a  $n$ -to- $2^n$  line decoder and  $m$  OR gates.

# Example Combinational Logic Implementation

- Implement a full adder using a decoder and OR gates.
- Truth table for full adder?

x	y	Z(carry from the previous lower significant position)	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = \sum (1,2,4,7)$$


$$C = \sum (3,5,6,7)$$

# Example ...

$$S = \sum (1,2,4,7)$$

$$C = \sum (3,5,6,7)$$

 - What do we need?
  - 3-to-8 line decoder
  - 2 OR gates



# ENCODERS

- Digital Circuit that performs the inverse operation of a decoder.
- Has  $2^n$  (or fewer) inputs and  $n$  output lines.
- The output lines generate the binary code corresponding to the input value.
- Ex: Octal-to-Binary encoder with the following truth table (it is assumed that only one input has a value of 1 at any given time.)

Inputs								Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$x$	$y$	$z$
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

- If two inputs are 1. How to resolve the ambiguity?
  - Define a priority rule for inputs.
- How to distinguish the case all inputs are 0 and  $D_0=1$ ?
  - Define an additional output which will be set when at least one input is 1.



# ENCODERS

- Priority Encoder: If two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence.

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

- V(valid bit) is set when one or more inputs are equal to 1.

# ENCODERS

- Priority Encoder example:

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

Karnaugh maps?

	00	01	11	10
00	X	1	1	1
01	0	1	1	1
11	0	1	1	1
10	0	1	1	1

	00	01	11	10
00				
01				
11				
10				

	00	01	11	10
00				
01				
11				
10				

# ENCODERS

- Priority Encoder example:

Inputs				Outputs		
$D_0$	$D_1$	$D_2$	$D_3$	$x$	$y$	$V$
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

Karnaugh maps?

	00	01	11	10
00	X	1	1	1
01	0	1	1	1
11	0	1	1	1
10	0	1	1	1

$$x = D_2 + D_3$$

	00	01	11	10
00	x	1	1	
01	1	1	1	
11	1	1	1	
10		1	1	

$$y = D_3 + D_1 D_2'$$

	00	01	11	10
00	0			
01				
11				
10				

$$V = D_0 + D_1 + D_2 + D_3$$


# ENCODERS

- Priority Encoder

$$x = D_2 + D_3$$



$$y = D_3 + D_1 D_2'$$

$$V = D_0 + D_1 + D_2 + D_3$$

 

  
# Multiplexers

- A multiplexer is a combinational circuit that selects Binary information from one of many input lines and directs it to a single output line.
- The selection of a particular input line is controlled by a set of selection lines.
- There are  $2^n$  input lines and  $n$  selection lines whose bit combinations determine which input is selected.
- Ex: a two-to-one-line multiplexer and its block diagram:


 
# Multiplexers


- Ex: A four-to-one-line multiplexer's logic diagram and function table:



$S_1$	$S_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

 
# Multiplexers

- A multiplexer is also called a selector, since it selects one of many inputs.
- A multiplexer may have an enable input to control the operation of the unit.
- A multiplexer can be constructed using a decoder.
  - Ex: a 4-to-1-line multiplexer can be constructed using a 2-to-4 line decoder and gates. How?


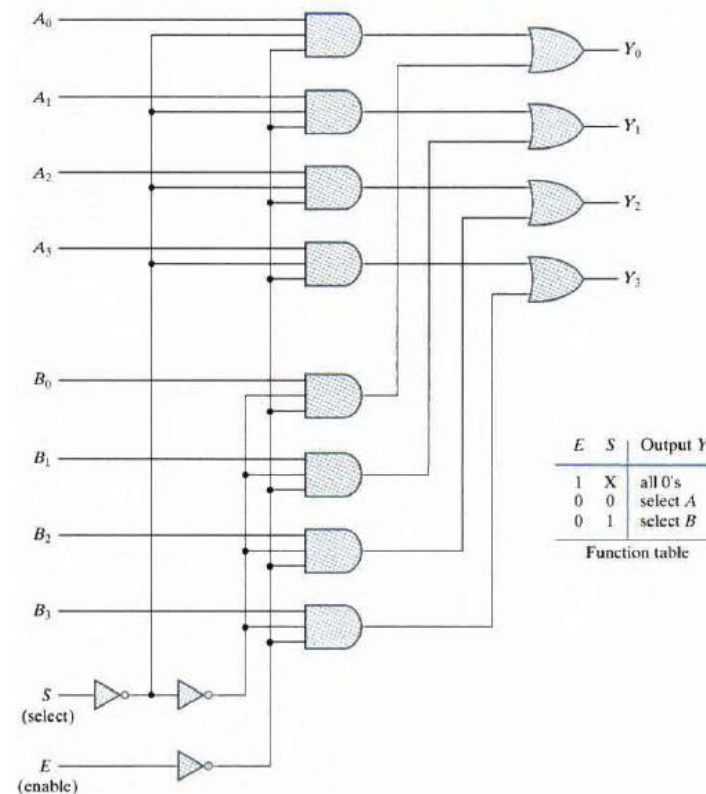
# Multiplexers


- Multiplexer circuits can be combined with common selection inputs to provide multiple-bit selection logic.
- Ex: A quadruple 2-to-1 line multiplexer's logic diagram and function table:




 
# Multiplexers

- Boolean Function implementation:
  - Previously we have seen how to use a decoder to implement a boolean function.
  - A multiplexer is a decoder that includes the OR gate within the unit.
    - The minterms of the function are generated in a multiplexer by the circuit associated with the selection inputs.
    - The individual minterms can be selected by the data inputs.
    - A boolean function with  $n$  variables can be implemented with a multiplexer that has  $n$  selection inputs and  $2^n$  data inputs, one for each minterm.



# Multiplexers


- Boolean Function implementation:
  - Boolean function of  $n$  variables can be implemented with a multiplexer that has  $n-1$  selection inputs.
  - The  $n-1$  variables of the function are connected to the selection inputs of the multiplexer.
  - The remaining single variable of the function is used for the data inputs.
  - If the single variable is  $z$ , each data of the multiplexer will be  $z, z', 1$  or  $0$ .

# Multiplexers

- Boolean Function implementation:
  - Ex:  $F(x,y,z) = \sum(1,2,6,7)$


x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

How to represent  
F using inputs?

 

 
# Multiplexers

- Boolean Function implementation:
  - Ex:  $F(x,y,z) = \sum(1,2,6,7)$



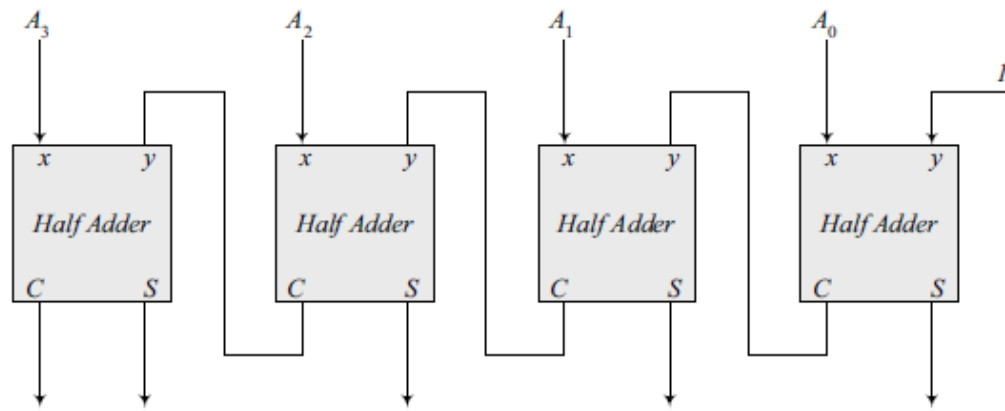
# Review questions

- Using half adders:
  - Design a four-bit combinational circuit incrementer (a circuit that adds 1 to a four-bit binary number)
  - Design a four-bit combinational circuit decrementer (a circuit that subtracts 1 from a four-bit binary number)





incrementer

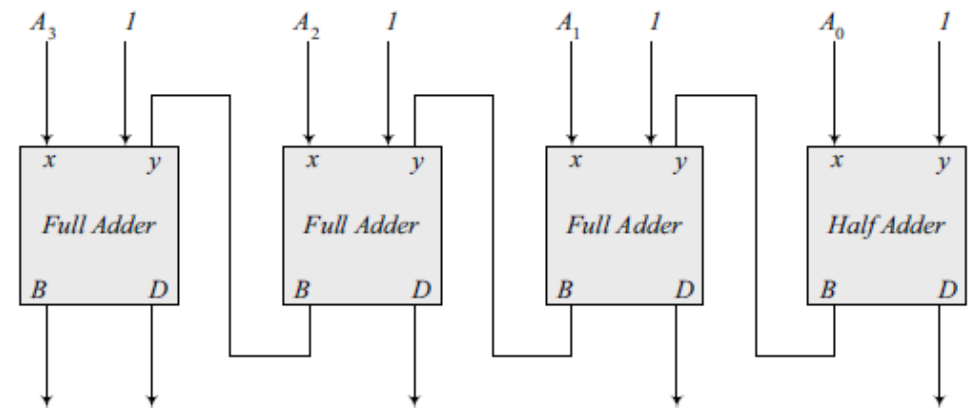

decrementer
  
# Review questions

- Construct a 16x1 multiplexer with two 8x1 and one 2x1 multiplexers. Use block diagrams.



$s_0$  —  
 $s_1$  —  
 $s_2$  —  
 $s_3$  —

—  $y$

