

# Digital Logic Systems – Registers, Counters and Memory Units- II

Assist. Prof. Özge ÖZTİMUR KARADAĞ

ALKÜ

# Previously..

- Synchronous sequential circuits for special purposes:
  - Registers
  - Counters
  - Memory Units
- Registers
  - Register with parallel load
  - Shift registers
  - Universal Shift Register

# Counters


- Two types of MSI Counters
  - Ripple Counters: a flip-flop output transition serves as a source for triggering other flip-flops.
    - the C input of some or all flip-flops are triggered not by the common clock pulses, but rather by the transition that occurs in other flip-flop outputs.
  - Synchronous Counters: the C input s of all flip -flops receive the common clock.

# Binary Ripple Counter

- A binary ripple counter consists of a series connection of complementing flip-flops with the output of each flip-flop connected to the C input of the next higher order flip-flop.
- The flip-flop holding the least significant bit receives the incoming count pulses
- A complementing flip-flop can be obtained from:
  - JK flip-flops by tying J and K inputs together.
  - T flip-flops
  - D flip-flop with the complement output connected to the *D* input.
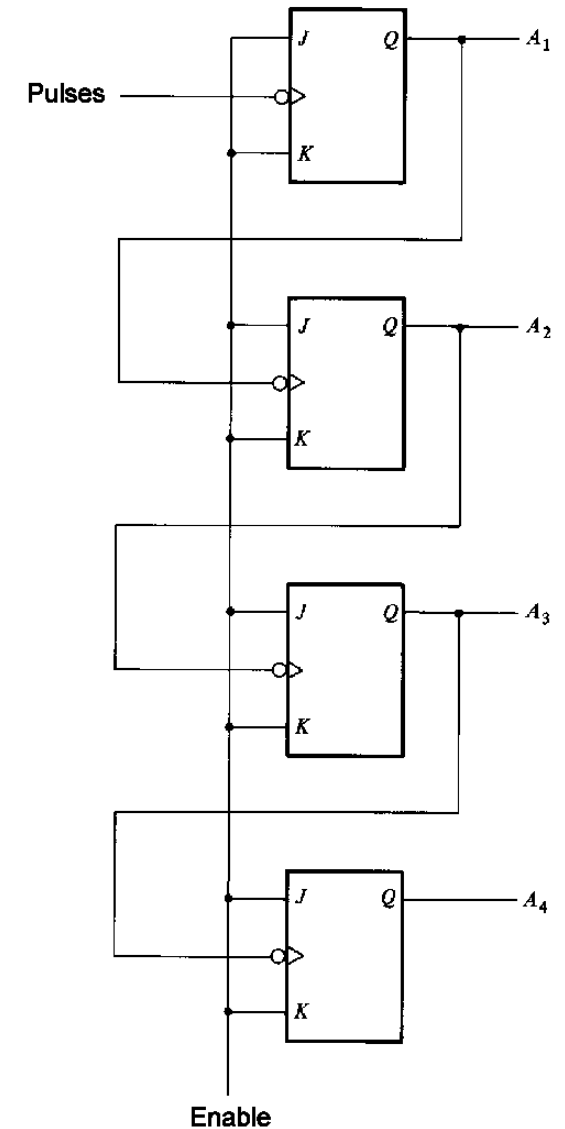
# Binary Ripple Counter


- 4 bit binary ripple counter:
  - JK inputs are 1. What does that mean?
    - Flip-flops will complement each time they are triggered.
  - Circle in the clock input implies that the flip-flop is negative edge triggered.



# Binary Ripple Counter

- Counting sequence:

Sayma Sırası					
$A_4$	$A_3$	$A_2$	$A_1$		
0	0	0	0	Complement of $A_1$	
0	0	0	1	Complement of $A_1$	$A_1$ 1 $\rightarrow$ 0, $A_2$ is complemented
0	0	1	0	Complement of $A_1$	
0	0	1	1	Complement of $A_1$	$A_1$ 1 $\rightarrow$ 0, $A_2$ is complemented
					$A_2$ 1 $\rightarrow$ 0, $A_3$ is complemented
0	1	0	0	Complement of $A_1$	
0	1	0	1	Complement of $A_1$	$A_1$ 1 $\rightarrow$ 0, $A_2$ is complemented
0	1	1	0	Complement of $A_1$	
0	1	1	1	Complement of $A_1$	$A_1$ 1 $\rightarrow$ 0, $A_2$ is complemented
					$A_2$ 1 $\rightarrow$ 0, $A_3$ is complemented
					$A_3$ 1 $\rightarrow$ 0, $A_4$ is complemented
1	0	0	0	...	

 

# Binary Ripple Counter


- The flip-flops change one at a time in succession, and the signal propagates through the counter in a ripple fashion from one stage to the next.
- Ripple counters are asynchronous counters.

# Ripple Counter

Binary Countdown Counter: A binary counter with a reverse count.

- the binary count is decremented by 1 with every input count pulse.
- The count of a four-bit countdown counter starts from binary 15 and continues to binary counts 14,13,12,...,0. and back to 15.
- If the outputs are obtained from  $Q'$  instead of  $Q$  then a binary countdown counter is obtained.
  - The least significant bit is complemented at each pulse.
  - Other bits are complemented when a previous bit goes from 0 to 1.
  - Either all flip-flops are positive edge triggered.
  - Or the  $C$  inputs of flip-flops are obtained from  $Q'$  of the previous flip-flop.

 
1111  
1110  
1101  
1100  
1011  
1010  
1001  
1000  
0111  
0110  
0101  
0100  
0011  
0010  
0001  
0000




 
# BCD Ripple Counter

- Decimal Counter 0-1-2-...-9-0
- How many flip-flops are required to represent a decimal?
  - 4
- State diagram?




# BCD Ripple Counter

- Logic circuit:
- What does this circuit tell?
  - When are the each Flip-flop triggered?
  - Do you remember the JK flip-flop characteristic table?


<b><i>JK Flip-Flop</i></b>			
<b><i>J</i></b>	<b><i>K</i></b>	<b><i>Q(t + 1)</i></b>	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

 - It is an asynchronous sequential circuit, can not be designed in the same way as the synchronous sequential circuits.



 
# BCD Ripple Counters

- State transition conditions for each flip-flop:
  1.  $Q_1$  is complemented at each negative edge of the count signal.
  2. If  $Q_8=0$  and  $Q_1$  goes from 1 to 0  $Q_2$  is complemented. If  $Q_8=1$  and  $Q_1$  goes from 1 to 0  $Q_2$  is reset to 0.
  3. If  $Q_2$  goes from 1 to 0  $Q_4$  is complemented.
  4. If  $Q_4Q_2=11$  and  $Q_1$  goes from 1 to 0  $Q_8$  is complemented. If either  $Q_4$  or  $Q_2$  is 0 and  $Q_1$  goes from 1 to 0  $Q_8$  is reset to 0.



 
# BCD Ripple Counter

- State transition conditions for each flip-flop:
  1.  $Q_1$  is complemented at each negative edge of the count signal.
  2. If  $Q_8=0$  and  $Q_1$  goes from 1 to 0  $Q_2$  is complemented. If  $Q_8=1$  and  $Q_1$  goes from 1 to 0  $Q_2$  is reset to 0.
  3. If  $Q_2$  goes from 1 to 0  $Q_4$  is complemented.
  4. If  $Q_4Q_2=11$  and  $Q_1$  goes from 1 to 0  $Q_8$  is complemented. If either  $Q_4$  or  $Q_2$  is 0 and  $Q_1$  goes from 1 to 0  $Q_8$  is reset to 0.



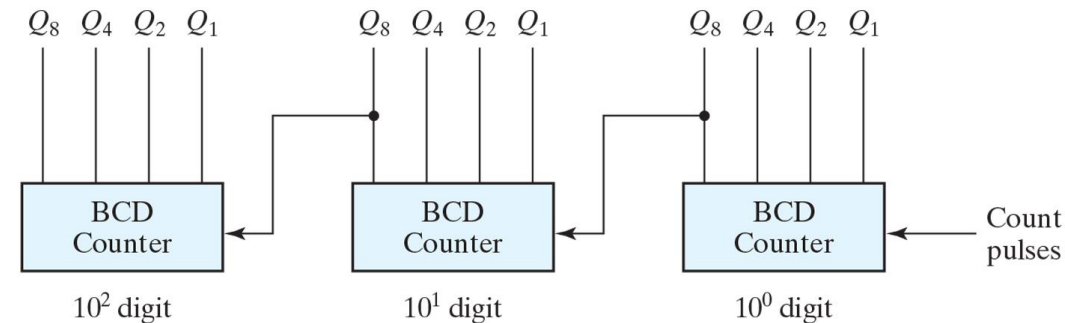
# BCD Ripple Counter

- The counter counts from 0 to 9.
- How to count from 0 to 99:
  - Need two bcd ripple counters
- How to count from 0 to 999:
  - Need three bcd ripple counters.
- Need as many counters as the number of digits.
- The  $Q_8$  output of the previous counter is applied as the count pulse to the counter at a higher digit.
- When  $Q_8$  goes from 1 to 0 the content of counter goes from 9 to 0 and the counter at the higher order is triggered to start counting.  
Example: 399 → 400


 
# Problem


- Which states are the unused states in a BCD Ripple Counter? Determine the next state for each of the unused state. Can the counter correct itself?
1.  $Q_1$  is complemented at each negative edge of the counr signal.
  2. If  $Q_8=0$  and  $Q_1$  goes from 1 to 0  $Q_2$  is complemented.  
If  $Q_8=1$  and  $Q_1$  goes from 1 to 0  $Q_2$  is reset to 0.
  3. If  $Q_2$  goes from 1 to 0  $Q_4$  is complemented.
  4. If  $Q_4Q_2=11$  and  $Q_1$  goes from 1 to 0  $Q_8$  is complemented. If either  $Q_4$  or  $Q_2$  is 0 and  $Q_1$  goes from 1 to 0  $Q_8$  is reset to 0.



# Problem..


- Unused states: 1010,1011,1100,1101,1110,1111
- Properties of the circuit:
  1.  $Q_1$  is complemented at each negative edge of the counr signal.
  2. If  $Q_8=0$  and  $Q_1$  goes from 1 to 0  $Q_2$  is complemented. If  $Q_8=1$  and  $Q_1$  goes from 1 to 0  $Q_2$  is reset to 0.
  3. If  $Q_2$  goes from 1 to 0  $Q_4$  is complemented.
  4. If  $Q_4Q_2=11$  and  $Q_1$  goes from 1 to 0  $Q_8$  is complemented. If either  $Q_4$  or  $Q_2$  is 0 and  $Q_1$  goes from 1 to 0  $Q_8$  is reset to 0.

Şimdiki Durum				Sonraki Durum			
Q8	Q4	Q2	Q1	Q8	Q4	Q2	Q1
1	0	1	0				
1	0	1	1				
1	1	0	0				
1	1	0	1				
1	1	1	0				
1	1	1	1				

 

- Can the counter correct itself?

Present State				Next State			
1	0	1	0	1	0	1	1
1	0	1	1	0	1	0	0
1	1	0	0	1	1	0	1
1	1	0	1	0	1	0	0
1	1	1	0	1	1	1	1
1	1	1	1	0	0	0	0

 



# References

- Morris Mano, Digital Design, 2nd edition