

# Digital Logic Systems – Algorithmic State Machines- I

Assist. Prof. Özge ÖZTİMUR KARADAĞ


ALKÜ

# Logic Design in Digital Systems

- Binary information in a digital system:
- **data**: discrete elements of information (binary words) that are manipulated by performing arithmetic, logic, shift, and other similar data-processing operations. These operations are implemented with digital components such as adders, decoders, multiplexers, counters, and shift registers.
- **control**: provides command signals that coordinate and execute the various operations in the data section in order to accomplish the desired data-processing tasks.
- The logic design of a digital system can be divided into two distinct parts:
  - the design of the digital circuits that perform the data-processing operations
  - the design of the control circuits that determine the sequence in which the various actions are performed
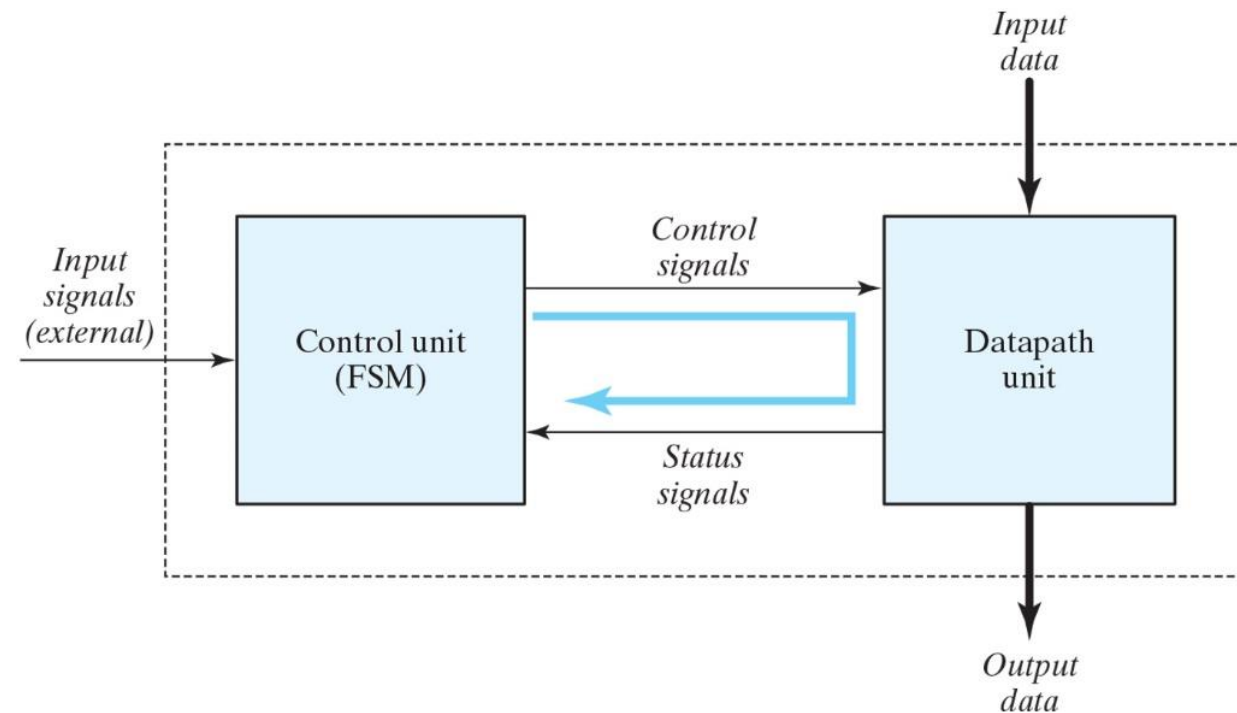
# Control Logic and the Datapath

- Interaction between the control logic and the datapath in digital systems:
- The *datapath unit*, manipulates data in registers according to the system's requirements
- *The control unit* issues a sequence of commands to the datapath unit.



# Control Logic

- generates the signals for sequencing the operations in the datapath unit
- is a finite state machine (FSM). i.e. a synchronous sequential circuit.
- Depending on status conditions and other external inputs the FSM goes to its next state to initiate other operations.

# Hardware Algorithm

- The control sequence and datapath tasks of a digital system are specified by means of a hardware algorithm.
- An algorithm consists of a finite number of procedural steps that specify how to obtain a solution to a problem.
- A hardware algorithm is a procedure for solving the problem with a given piece of equipment.
- The most challenging and creative part of digital design is the formulation of hardware algorithms for achieving required objectives

# Hardware Algorithm

- How to represent an algorithm?
  - A flowchart is a convenient way to specify the sequence of procedural steps and decision paths for an algorithm.
- Algorithmic State Machine(ASM) Chart: flowchart that has been developed specifically to define digital hardware algorithms.
- State Machine: Another term for a sequential circuit which is the basic structure of a digital system.

# Algorithmic State Machines(ASM)

- A conventional flowchart that describes the procedural steps and decision paths of an algorithm in a sequential manner, without taking into consideration their time relationship.
- The ASM chart describes the sequence of events, as well as the timing relationship between the states of a sequential controller and the events that occur while going from one state to the next (i.e., the events that are synchronous with changes in the state).
- How is the ASM used for design?
  - Let's introduce its parts.



# ASM Chart

- A special flowchart for representing sequential processes in a digital system.
- Three main items:
  - State box
  - Decision box
  - Conditional box



  
# ASM Chart

- State Box
  - a) general representation
  - b) example





 
# ASM Chart

- Decision Box describes the effect of an input (i.e. • a primary, or external, input or a status. or internal, signal) on the control subsystem.
  - Input to be tested is placed in the box.



  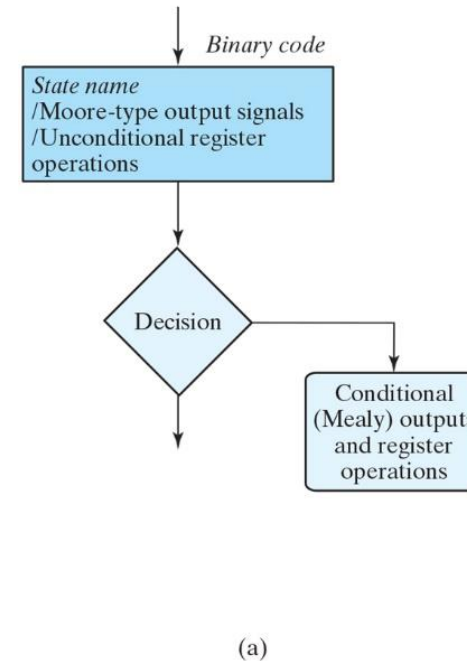
# ASM Chart

- Conditional Box:
  - Has rounded corner.
  - The input path to the conditional box must come from one of the exit paths of a decision box.
  - The outputs listed inside the conditional box are generated as Mealy-type signals during a given state; the register operations listed in the conditional box are associated with a transition from the state.
- a) general representation
- b) sample (data path and control)
- c) sample (control)




 
# ASM Chart

- ASM Block: An ASM block is a structure consisting of one state box and all the decision and conditional boxes connected to its exit path.
- An ASM block has one entrance and any number of exit paths represented by the structure of the decision boxes.
- An ASM chart consists of one or more interconnected blocks.
- A state box without any decision or conditional boxes constitutes a simple block.
- **Each block in the ASM chart describes the state of the system during one clock-pulse interval.**
- The operations within the state and conditional boxes initiated by a common clock pulse when the state of the controller transitions from  $S\_0$  to its next state. The same clock pulse transfers the system controller to one of the next states,  $S\_1$ ,  $S\_2$ , or  $S\_3$ , as dictated by the binary values of  $E$  and  $F$ .


  
# ASM Chart

- The ASM chart is similar to a state diagram.
- Each state block is equivalent to a state in a sequential circuit.
- The decision box is equivalent to the binary information written along the directed lines that connect two states in a state diagram.



# ASM Chart

- Symbolic representation of register operations


Symbolic Representation	Definition
$A \leftarrow B$	Transfer content of B to register A.
$R \leftarrow 0$	Reset R
$F \leftarrow 1$	Set F
$A \leftarrow A+1$	Count up A
$A \leftarrow A-1$	Count down A
$A \leftarrow A+B$	Add content of register B to A

# Considering the Timing

- All the registers and flip-flops are controlled with a single clock generator.
- Clock signals are applied to all registers in datapath and control logic.
- It is assumed that all clock signals are synchronized and all flip-flops are positive edge triggered.
- The difference between a classical flow chart and an algorithmic state machine is the interpretation about the timing.
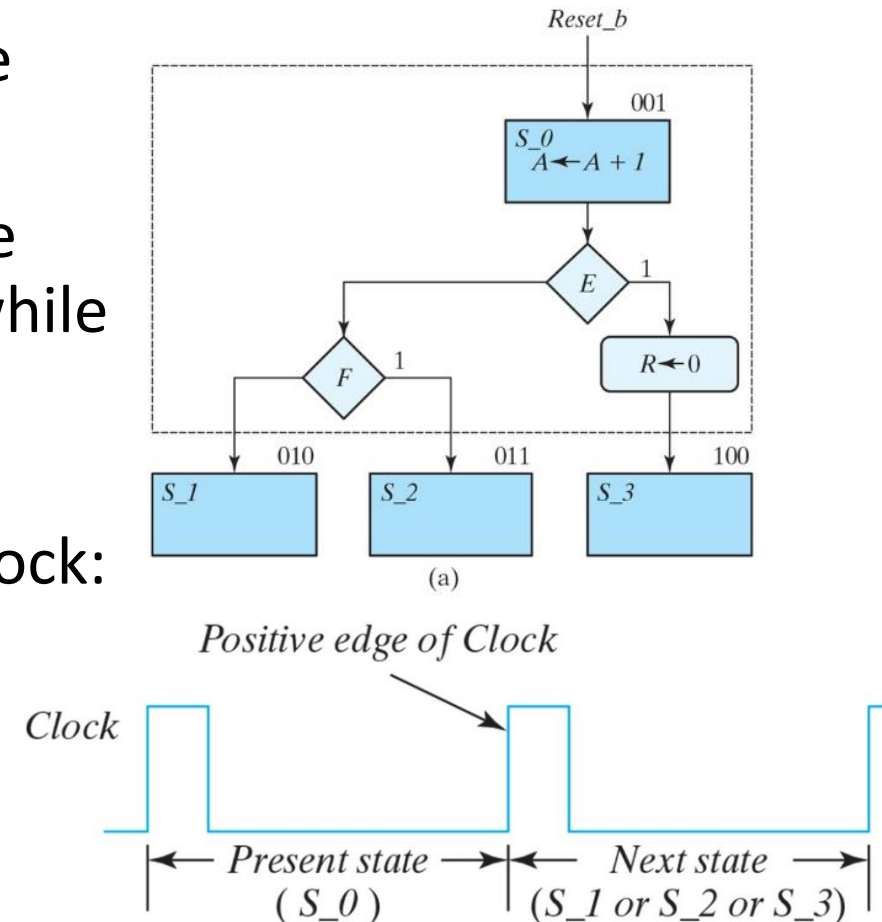
# Considering the Timing

- If this was a regular flow chart, processes could be assumed to be successive.
- An ASM block is considered as a single unit. All the processes in the block take place synchronously while the system goes from state  $S_0$  to the next state.
- In the example, the following operations occur **simultaneously** at the next positive edge of the clock:
  - Register  $A$  is incremented.
  - If  $E=1$  register  $R$  is cleared.
  - Control transfers to the next state.






# Design Example

- We want to design a digital system with two flip-flops; E and F and a 4 bit binary counter A.
- Flip-flops in A are  $A_4, A_3, A_2, A_1$ . ( $A_4$  for the most significant bit)
- A signal  $S$ , initiates the system's operation by clearing the counter A and flip- flop  $F$ .
- At each subsequent clock pulse the counter is incremented by 1 until the operations stop.
- $A_3$  and  $A_4$  determine the sequence of operations:
  - If  $A_3=0$  E is cleared to 0 and count continues.
  - If  $A_3=1$  E is set to 1; then if  $A_4=0$  the count continues, if  $A_4=1$  F is set to 1 on the next clock pulse and the system stops counting.
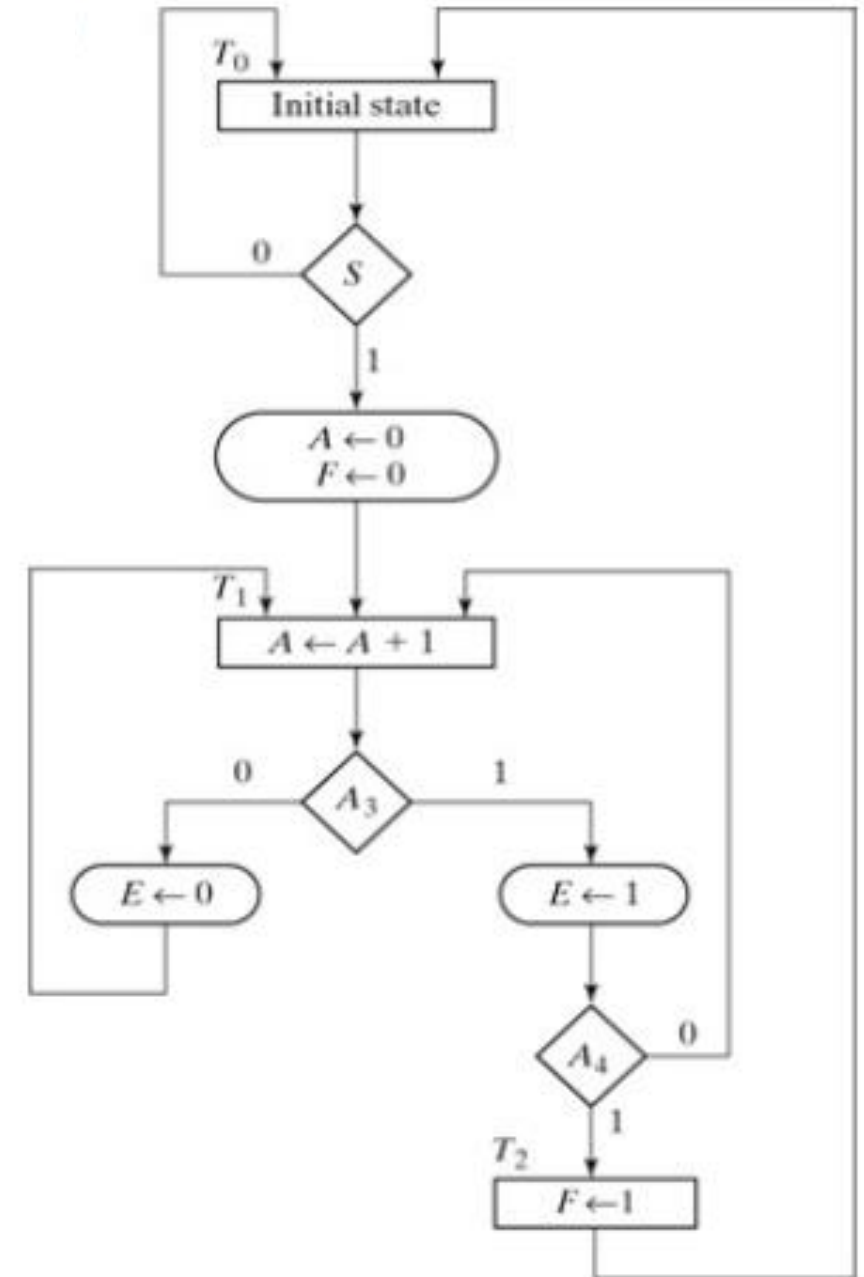
# Design Example...


- We want to design a digital system with two flip-flops; E and F and a 4 bit binary counter A.
- Flip-flops in A are  $A_4, A_3, A_2, A_1$ . ( $A_4$  for the most significant bit)
- A signal  $S$ , initiates the system's operation by clearing the counter  $A$  and flip-flop  $F$ .
- At each subsequent clock pulse the counter is incremented by 1 until the operations stop.
- $A_3$  and  $A_4$  determine the sequence of operations:
  - If  $A_3=0$  E is cleared to 0 and count continues.
  - If  $A_3=1$  E is set to 1; then if  $A_4=0$  the count continues, if  $A_4=1$  F is set to 1 on the next clock pulse and the system stops counting.




# Design Example...

- Zama

Counter				Flip-flops		Conditions	State
A4	A3	A2	A1	E	F		
0	0	0	0	1	0	A3=0, A4=0	T <sub>1</sub>
0	0	0	1	0	0		
0	0	1	0	0	0		
0	0	1	1	0	0		
0	1	0	0	0	0	A3=1, A4=0	
0	1	0	1	1	0		
0	1	1	0	1	0		
0	1	1	1	1	0		
1	0	0	0	1	0	A3=0, A4=1	
1	0	0	1	0	0		
1	0	1	0	0	0		
1	0	1	1	0	0		
1	1	0	0	0	0		
1	1	0	1	1	0		T <sub>2</sub>
1	1	0	1	1	1		T <sub>0</sub>

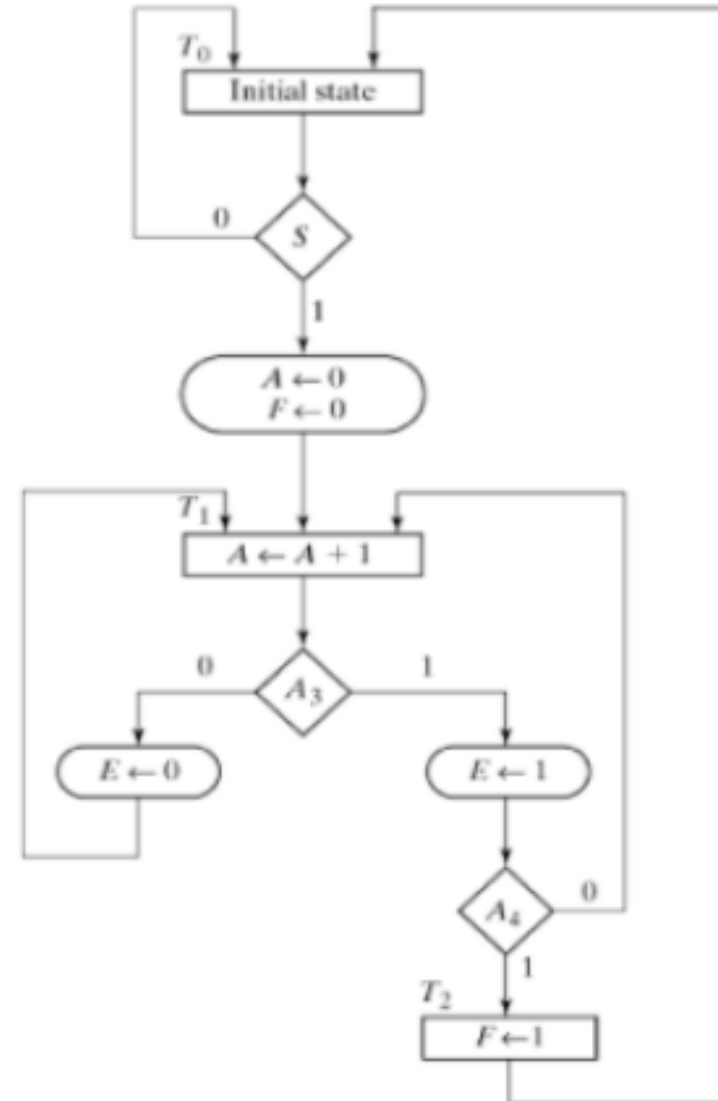

- Datapath

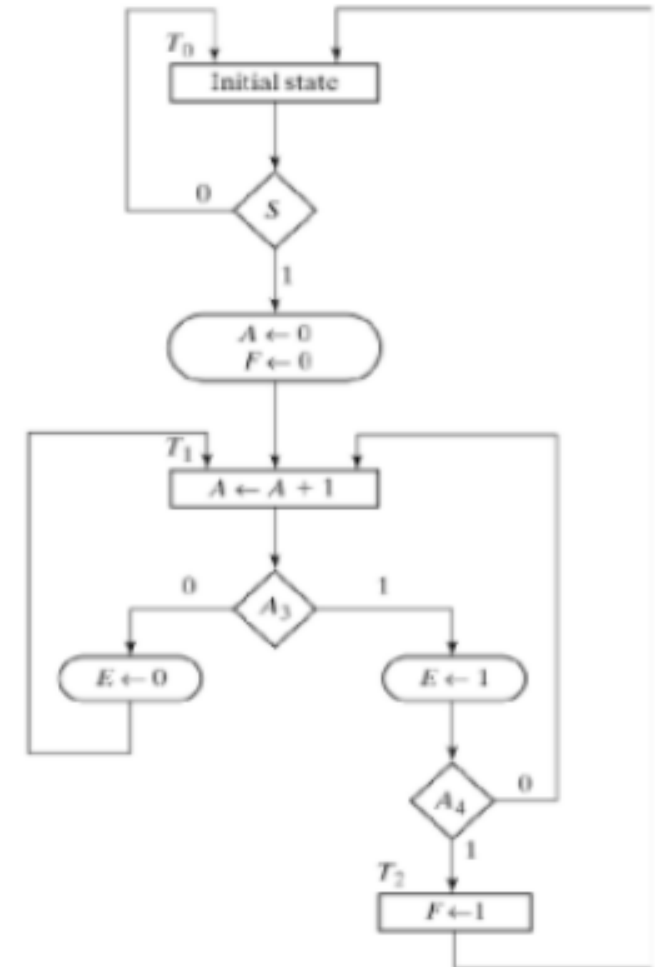

# References

- Morris Mano, Digital Design