 


# Digital Logic Systems— Synchronous Sequential Logic- II

Assist. Prof. Özge ÖZTİMUR KARADAĞ


ALKÜ

# Block Diagram of Sequential Circuit



- Memory Elements
  - Store binary data.
  - This data is referred as the current state of the flip-flop.
- Sequential Circuit
  - Determines the output using input and the current state.
  - Input and the current state determine the next state.

# Synchronous Sequential Circuit

 

(a) Block diagram




(b) Timing diagram of clock pulses

# Flip-Flops

- A flip-flop can hold its state until an input signal is asserted to change its state.
- Types of Flip-flops vary:
  - By the number of input signals.
  - How the inputs effect the binary state of the flip-flop.

# A Simple Flip-flop Circuit

x	y	x NOR y
0	0	1
0	1	0
1	0	0
1	1	0

 

(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	1	0
0	0	1	0 (after $S = 1, R = 0$ )
0	1	0	1
0	0	0	1 (after $S = 0, R = 1$ )
1	1	0	0 (forbidden)

(b) Function table


Q state of the flip-flop, Q' complement of Q.

Q=1, Q'=0 set

Q=0, Q'=1 reset

# Flip-Flop with NAND Gates

x	y	x NAND y
0	0	1
0	1	1
1	0	1
1	1	0

 

(a) Logic diagram

$S$	$R$	$Q$	$Q'$
1	0	0	1
1	1	0	1 (after $S = 1, R = 0$ )
0	1	1	0
1	1	1	0 (after $S = 0, R = 1$ )
0	0	1	1 (forbidden)

(b) Function table

# RS Flip-Flop

	00	01	11	10
0			X	1
1	1		X	1


$$Q(t+1) = S + R'Q$$

$$SR = 0$$

Characteristic Equation

Q	S	R	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	Indetermined
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	Indetermined

Characteristic Table

 

(a) Logic diagram

En	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate

(b) Function table


# D Flip-Flop

Q	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

Characteristic Table

	0	1
0		1
1		1

$Q(t+1)=D$   
Characteristic Equation

 


(a) Logic diagram

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$ ; reset state
1	1	$Q = 1$ ; set state


(b) Function table




# J-K Flip-Flop

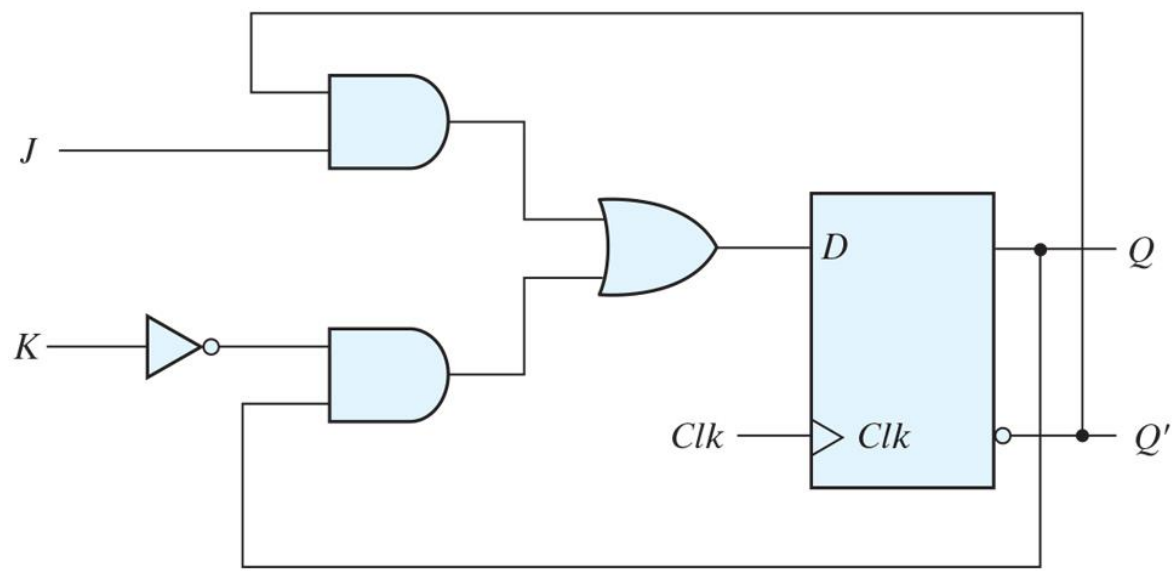

(a) Circuit diagram

 

(b) Graphic symbol

 


Characteristic Equation


Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Characteristic Table


# T Flip-Flop

 

(a) From JK flip-flop

 


(b) From D flip-flop

 

(c) Graphic symbol




Q	T	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

Characteristic Table

 


Characteristic Equation


# Graphical Symbols of Flip-Flops

   
 
# Graphical Representation of Edge Triggered D Flip-Flops



(a) Positive-edge

 

(b) Negative-edge

# Flip-Flop Characteristic Tables

<b><i>JK</i> Flip-Flop</b>			
<b><i>J</i></b>	<b><i>K</i></b>	<b><math>Q(t + 1)</math></b>	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

<b><i>D</i> Flip-Flop</b>		
<b><i>D</i></b>	<b><math>Q(t + 1)</math></b>	
0	0	Reset
1	1	Set

<b><i>T</i> Flip-Flop</b>		
<b><i>T</i></b>	<b><math>Q(t + 1)</math></b>	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

# Flip-Flop and Clock Signal

- If flip-flops respond to a **level of clock**, indetermined conditions may arise.
  - If the flip-flop outputs change while the output of the combinational circuit which are fed as input to flip flops then indetermined condition arises.
- Solution: Flip-flops respond to **clock transitions**..



(a) Response to positive level



(b) Positive-edge response




(c) Negative-edge response

# Analysis of Clocked Sequential Circuits

- Analysis describes what a given circuit will do under certain operating conditions.
- Obtain a table or a diagram for the time sequence of inputs, outputs and internal states.
- An algebraic representation for specifying the next-state condition in terms of the present state and inputs.
- **State Equations:** specifies the next state as a function of the present state and inputs.

# Example of a Sequential Circuit

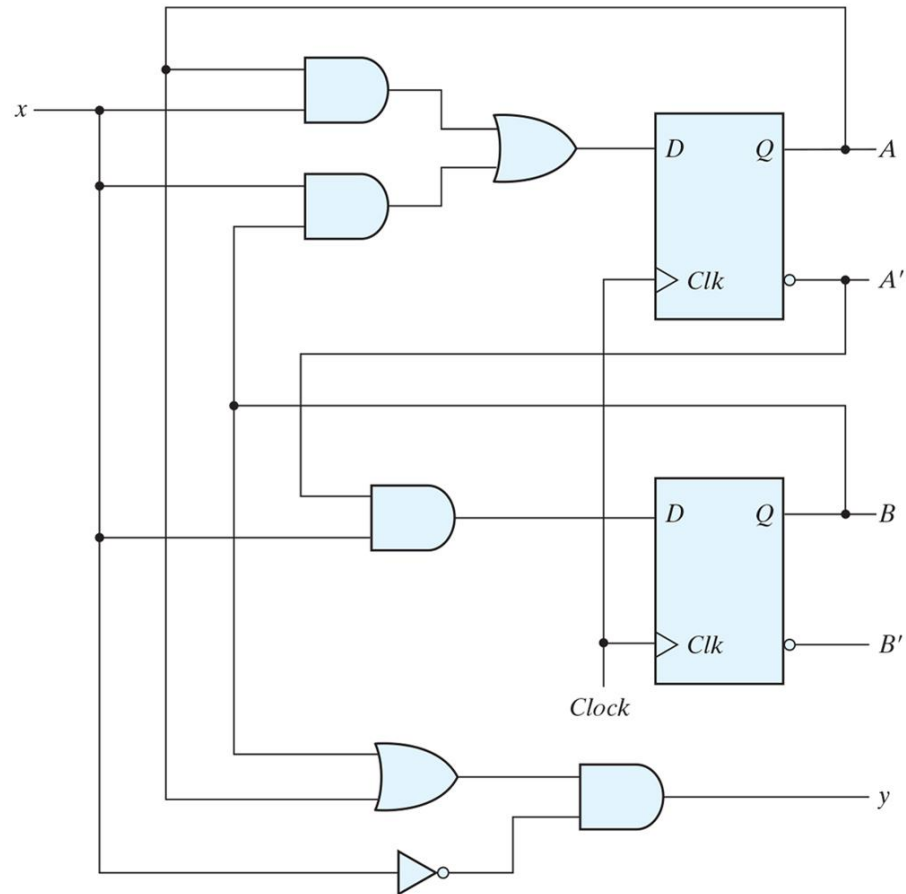

- State Equations?

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

$$y = (A + B)x'$$

- State Table?



# State Table- 1

$$A(t + 1) = Ax + Bx$$

$$B(t + 1) = A'x$$

$$y = (A + B)x'$$

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Present State		Input	Next State		Output
<i>A</i>	<i>B</i>	<i>x</i>	<i>A</i>	<i>B</i>	<i>y</i>
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


# State Table- 2

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>y</i>	<i>y</i>
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

# State Diagram

- How many states ?
- How to represent transitions between states?

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>A</i>	<i>B</i>	<i>y</i>	<i>y</i>
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

 


# Flip-Flop Input Equations

- *What is the input equation for a D flip-flop which comes from an output of an OR gate with inputs  $x$  and  $y$ ?*
  - $D_Q = x + y$
 
# Analysis with D Flip-Flop

$A(t+1) = A \text{ xor } (x \text{ xor } y)$



(a) Circuit diagram

Blank state table placeholder.

(b) State table




(c) State diagram

Present State	Inputs		Next State
A	x	y	A
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

# Analysis with JK Flip-Flop

JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

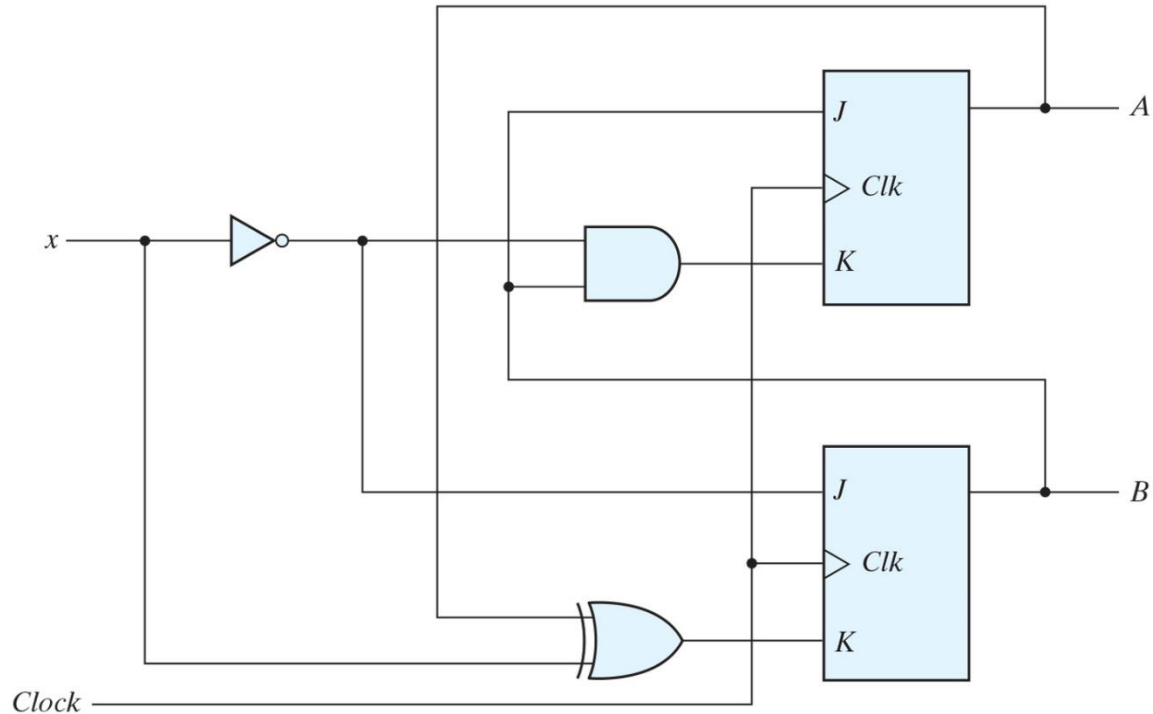

$$J_A = B$$

$$K_A = x'B$$

$$J_B = x'$$

$$K_B = A \text{ xor } x$$

## • State Table

Present State		Input	Next State		Flip-Flop Inputs			
A	B	x	A	B	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>
0	0	0						
0	0	1						
0	1	0						
0	1	1						
1	0	0						
1	0	1						
1	1	0						
1	1	1						






# Analysis with JK Flip-Flop..

- State Diagram
  - From state diagram to state table


Present State		Input	Next State		Flip-Flop Inputs			
A	B		A	B	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

 

# Analysis with T Flip-Flop

## T Flip-Flop


$T$	$Q(t + 1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

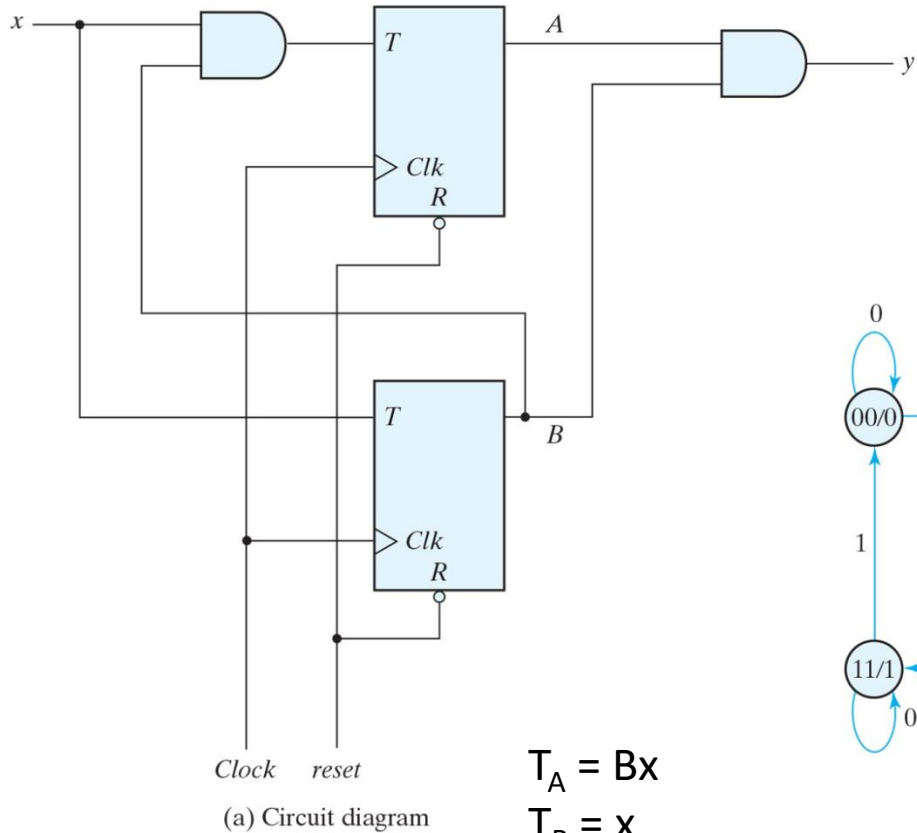

$$T_A = Bx$$

$$T_B = x$$

$$y = AB$$


 


## • State Table

Present State		Input $x$	Next State		Output $y$	$T_A$	$T_B$
$A$	$B$		$A$	$B$			
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

Present State		Input	Next State		Output
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

# Mealy and Moore Models

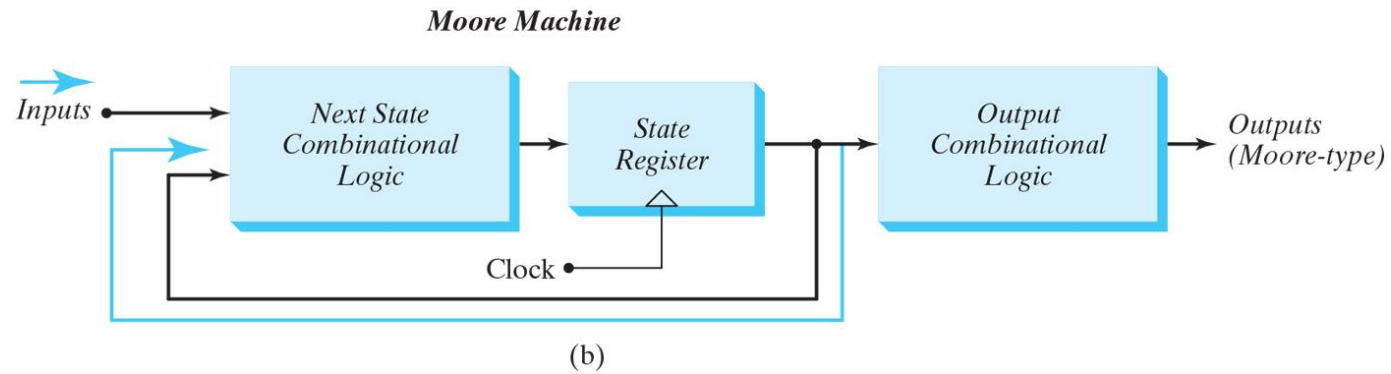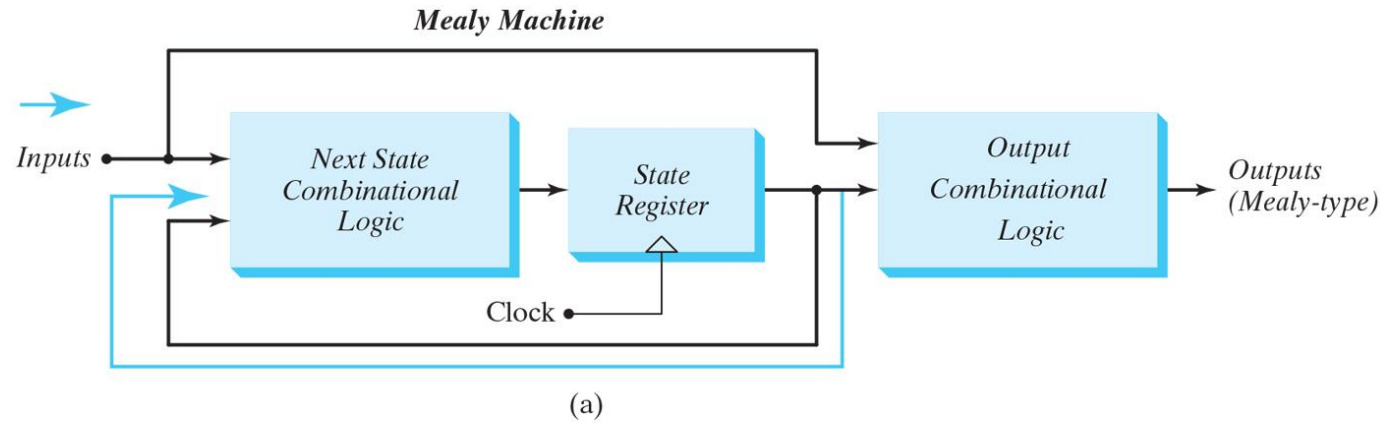

- Questions ?
- Comments ?

# References

- Morris Mano, Digital Design