

Digital Logic Systems – Synchronous Sequential Logic - III

Assist. Prof. Özge ÖZTİMUR KARADAĞ
ALKÜ

Previously..

- Analysis of Synchronous Sequential Circuit
 - Circuit → State Table / Diagram
 - State Reduction
 - State Assignment
 - Flip-flop excitation tables
- Design of Synchronous Sequential Circuit
 - Design of a circuit whose behaviour is described by text..
 - Design of a circuit whose state diagram is given..
 - An example with JK Flip-flops.

Example

- Given the state table, design the corresponding sequential circuit using D flip-flops:

- Flip-flop inputs as sum of products:

- $DA(A, B, x) = \sum(2, 4, 5, 6)$

	00	01	11	10
0				1
1	1	1		1

$$= AB' + Bx'$$

- $DB(A, B, x) = \sum(1, 3, 5, 6)$

	00	01	11	10
0		1	1	
1		1		1

$$= A'x + B'x + ABx'$$

- $y = \sum(1, 5)$

	00	01	11	10
0		1		
1		1		

$$= B'x$$

Current State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

Design with Unused States

- There will be 2^m possible states with m flip-flops.
- But there can be unused states.
- Unused states are considered as **don't care conditions**.

Example

Q(t)	Q(t+1)	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

S	R	Q(t+1)	R
0	0	Q(t)	No chnage
0	1	0	Reset
1	0	1	Set
1	1	?	0

Current State			Input	Next State			Flip-flop Inputs						Output
A	B	C	x	A	B	C	SA	RA	SB	RB	SC	RC	y
0	0	1	0	0	0	1							0
0	0	1	1	0	1	0							0
0	1	0	0	0	1	1							0
0	1	0	1	1	0	0							0
0	1	1	0	0	0	1							0
0	1	1	1	1	0	0							0
1	0	0	0	1	0	1							0
1	0	0	1	1	0	0							1
1	0	1	0	0	0	1							0
1	0	1	1	1	0	0							1


Example...

- Unused States:
 - 000,110,111

Şimdiki durum			Gir iş	Sonraki durum			Flip-flop girişleri						çık iş
A	B	C	x	A	B	C	SA	RA	SB	RB	SC	RC	y
0	0	1	0	0	0	1	0	X	0	X	X	0	0
0	0	1	1	0	1	0	0	X	1	0	0	1	0
0	1	0	0	0	1	1	0	X	X	0	1	0	0
0	1	0	1	1	0	0	1	0	0	1	0	X	0
0	1	1	0	0	0	1	0	X	0	1	X	0	0
0	1	1	1	1	0	0	1	0	0	1	0	1	0
1	0	0	0	1	0	1	X	0	0	X	1	0	0
1	0	0	1	1	0	0	X	0	0	X	0	X	1
1	0	1	0	0	0	1	0	1	0	X	X	0	0
1	0	1	1	1	0	0	X	0	0	X	0	1	1


Combinational Circuit:

- SA,RA,SB,RB,SC,RC,y

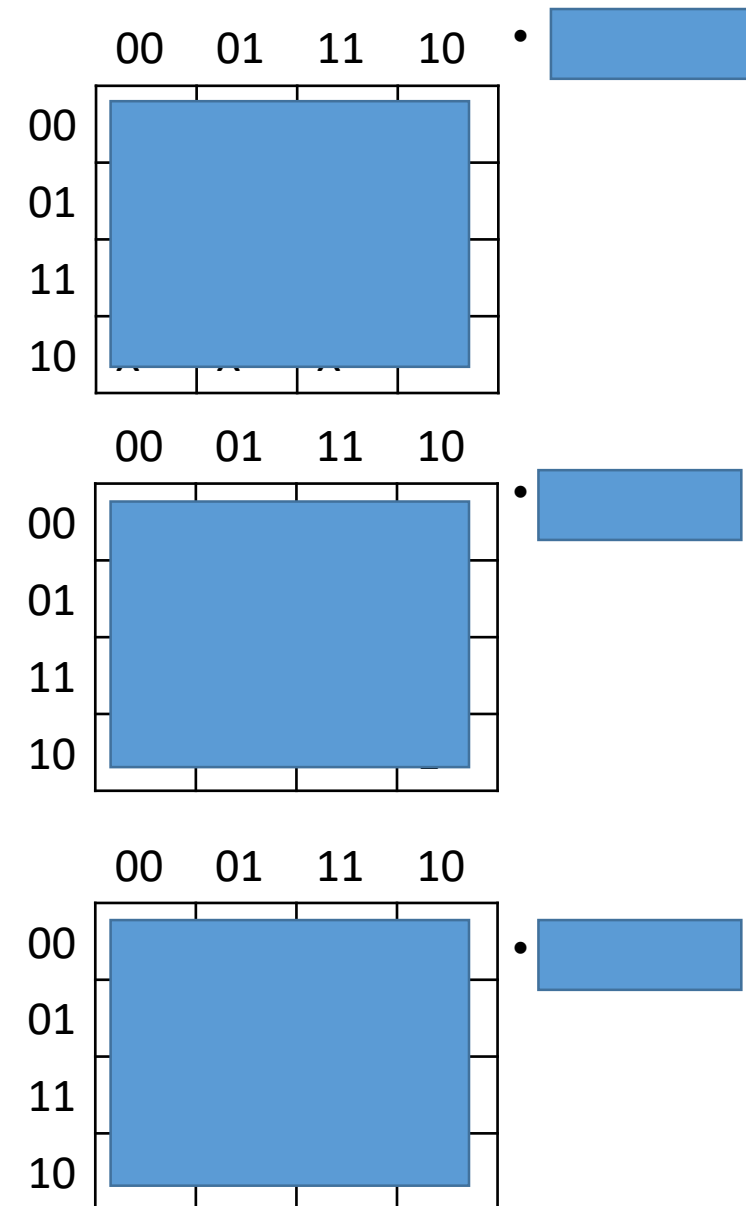


Example...


Current State			Input	Next State			Flip-flop inputs						output
A	B	C	x	A	B	C	SA	RA	SB	RB	SC	RC	y
0	0	1	0	0	0	1	0	X	0	X	X	0	0
0	0	1	1	0	1	0	0	X	1	0	0	1	0
0	1	0	0	0	1	1	0	X	X	0	1	0	0
0	1	0	1	1	0	0	1	0	0	1	0	X	0
0	1	1	0	0	0	1	0	X	0	1	X	0	0
0	1	1	1	1	0	0	1	0	0	1	0	1	0
1	0	0	0	1	0	1	X	0	0	X	1	0	0
1	0	0	1	1	0	0	X	0	0	X	0	X	1
1	0	1	0	0	0	1	0	1	0	X	X	0	0
1	0	1	1	1	0	0	X	0	0	X	0	1	1

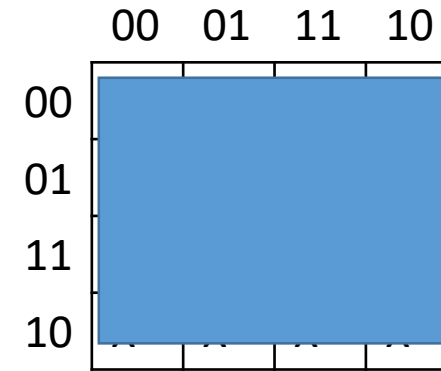


• RB =

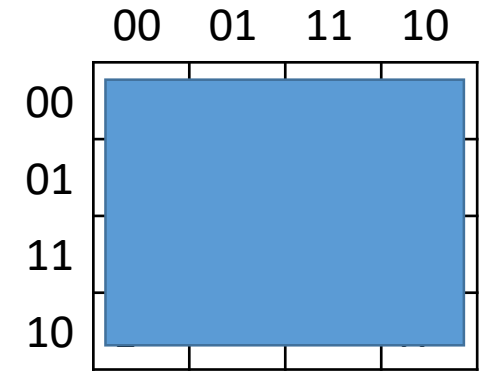

SC =

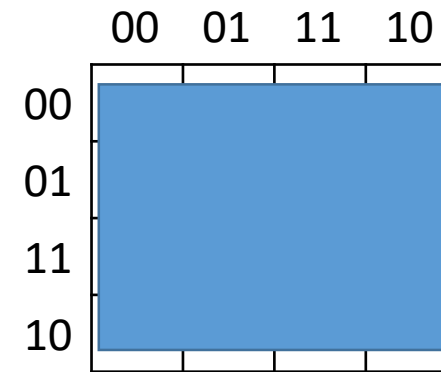

• RC =

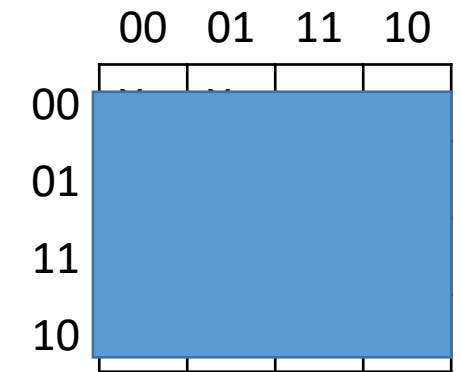


y =

Initial State of Sequential Circuits

- It is not possible to know in advance in which state the circuit will be when the energy is given.
- In general, a reset or set is applied to all flip-flops in the beginning.
- In order to be sure that the circuit is not stuck in some unused state, it is safe to put the circuit in an initial state.

Design of Counters

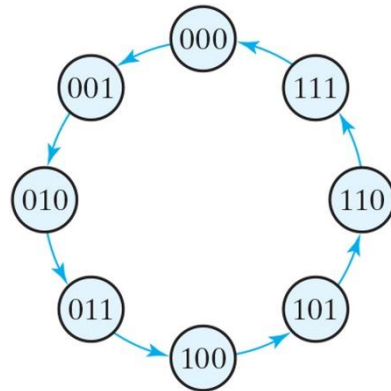
- A counter is a sequential circuit which goes through previously defined states as input signal is applied.
- State diagram of a 3 bit binary counter:
 - Note that the arrows are not signed with input/output values.



Design of Counter

Q(t)	Q(t+1)	T	T		Q(t+1)	
0	0	0	0	Q(t)	No change	
0	1	1				
1	0	1	1	Q'(t)	Complement	
1	1	0				

- 3 bit binary counter

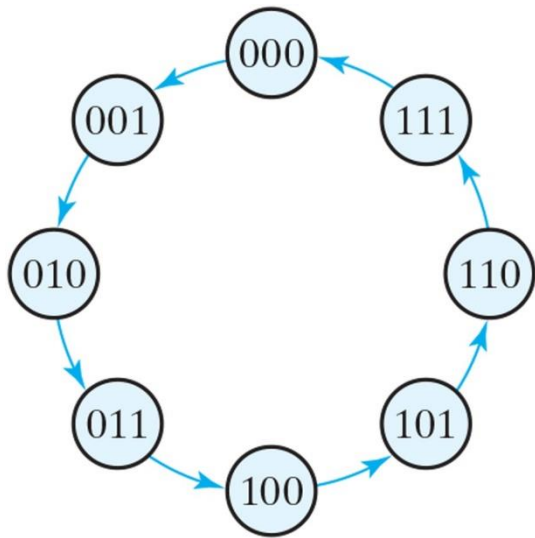

- Excitation Table?

Current State			Next State			Flip-flop Inputs		
A2	A1	A0	A2	A1	A0	TA2	TA1	TA0
0	0	0	0	0	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
0	0	1	0	1	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
0	1	0	0	1	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
0	1	1	1	0	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	0	0	1	0	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	0	1	1	1	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	1	0	1	1	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	1	1	0	0	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Desing of Counter

- Flip-flop input functions?


Current State			Next State			Flip-flop Inputs		
A2	A1	A0	A2	A1	A0	TA2	TA1	TA0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

TA2 ?

TA1 ?

TA0 ?

Design of Counter

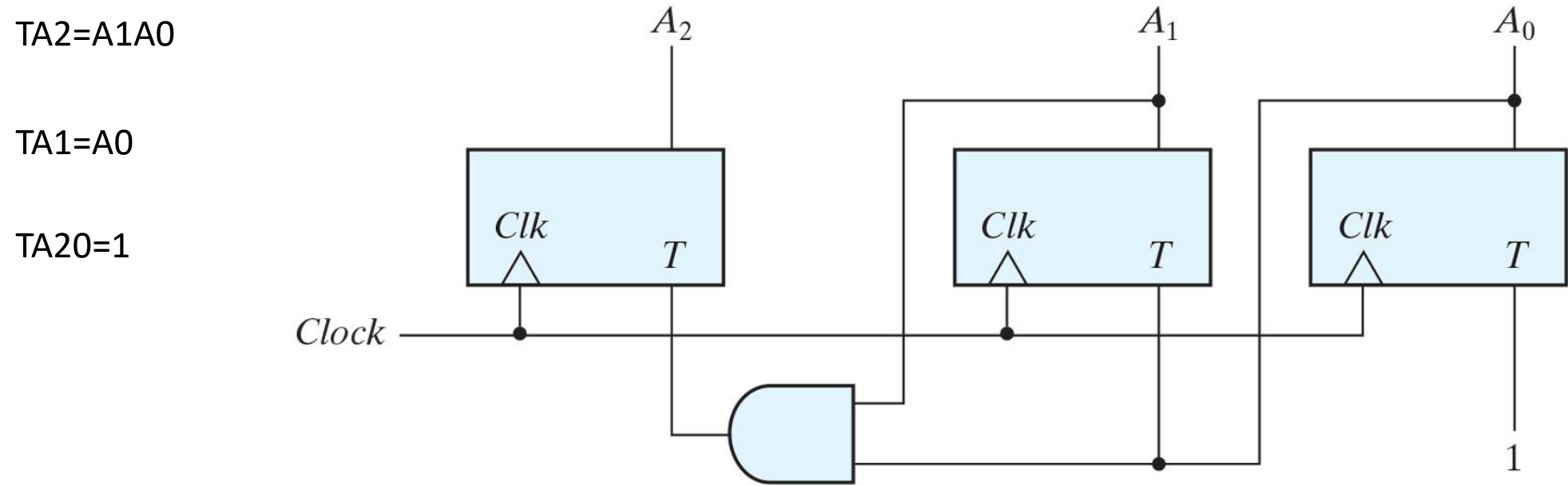

Other Counters

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

J	K	Q(t+1)	R
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t+1)	0

- A counter with n flip-flops may have less than 2^n number of states.
- Ex:

Current State			Next State			Flip-flop inputs					
A	B	C	A	B	C	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1						
0	0	1	0	1	0						
0	1	0	1	0	0						
1	0	0	1	0	1						
1	0	1	1	1	0						
1	1	0	0	0	0						

Ex: Other Counters

- Flip-flop inputs:


- $JA=B$ $KA=B$
- $JB=C$ $KB=1$
- $JC=B'$ $KC=1$

Current state			Sonraki durum			Flip-flop girişleri					
A	B	C	A	B	C	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

- What happens when the circuit is in state 011?

- $JA=KA=1$
- $JB=KB=1$
- $JC=0, KC=1$
- Next State: 100

State Diagram of the Counter:

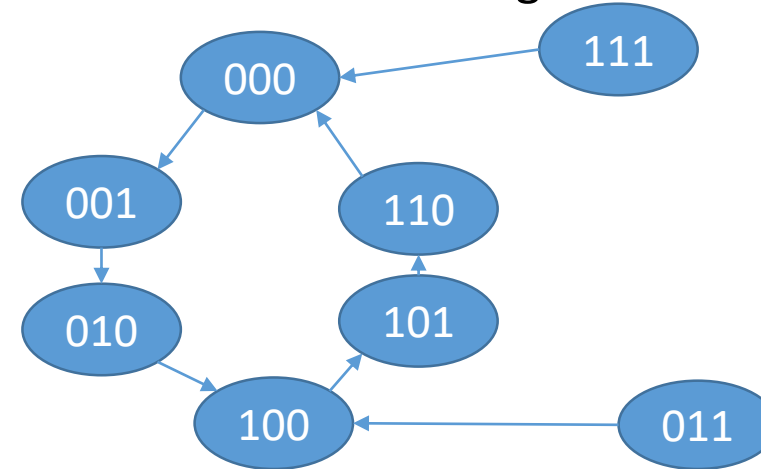


Problem

- A sequential circuit with two D flip-flops A and B, two inputs x and y and an output z is defined with the following next state and output functions:
 - $A(t+1) = x'y + xA$
 - $B(t+1) = x'B + xA$
 - $z = B$
- Draw the logic diagram for this circuit.
- Write the state table.
- Draw the state diagram.

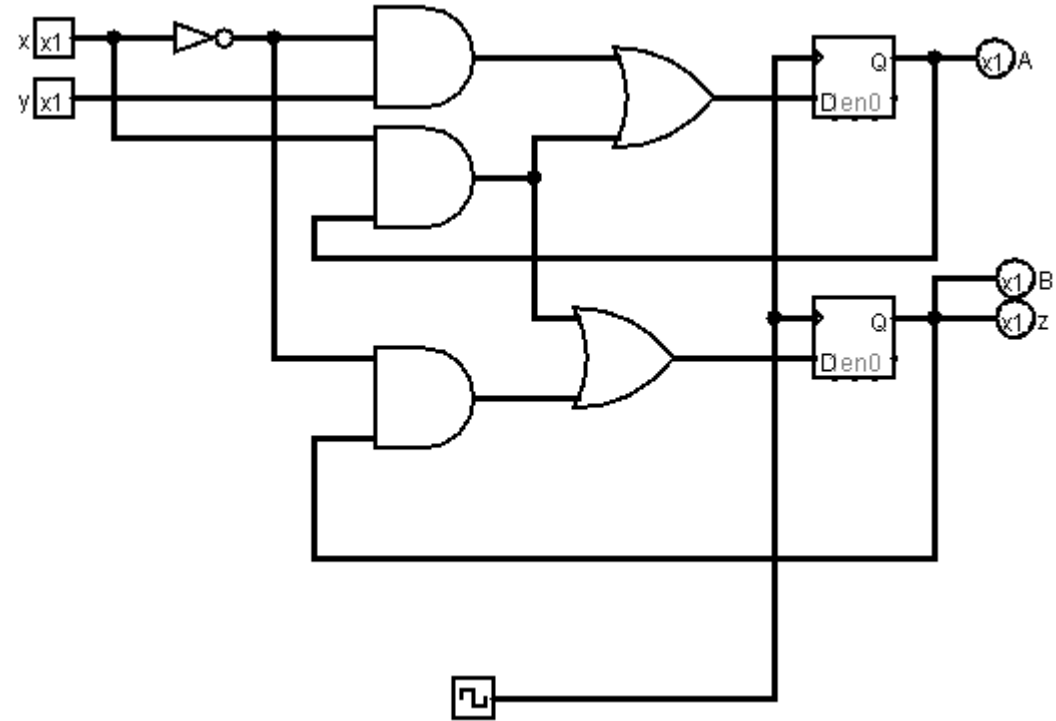Problem...

- $A(t+1) = x'y + xA$
- $B(t+1) = x'B + xA$
- $z = B$
- The logic diagram of the circuit:



Problem...

- State Table

$$A(t+1) = x'y + xA$$

$$B(t+1) = x'B + xA$$


$$z = B$$

Present State		Inputs		Next State		Output
A	B	x	y	A	B	z
0	0	0	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
0	0	0	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
0	0	1	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
0	0	1	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
0	1	0	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
0	1	0	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
0	1	1	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
0	1	1	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	0	0	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	0	0	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	0	1	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	0	1	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	1	0	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	1	0	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	1	1	0	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
1	1	1	1	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Problem...

- State Diagram:

<i>Present state</i>		<i>Inputs</i>		<i>Next state</i>		<i>Output</i>
<i>A</i>	<i>B</i>	<i>x</i>	<i>y</i>	<i>A</i>	<i>B</i>	<i>z</i>
0	0	0	0	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	1	1
0	1	0	1	1	1	1
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

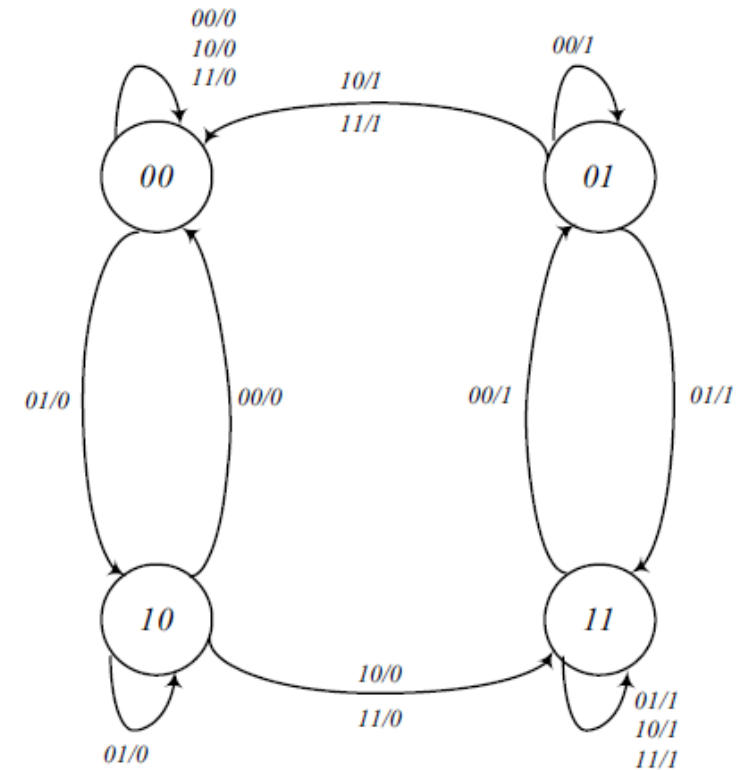

References

- Morris Mano, Digital Design.