

# COM 205 - Digital Logic Design

## Boolean Algebra and Logic Gates


### -VI

Assist. Prof. Özge ÖZTİMUR KARADAĞ  
ALKÜ


# Last Week

- Implementation of the function in a standard form is said to be a two-level implementation

a.  $F = B'D' + B'C' + A'C'D$


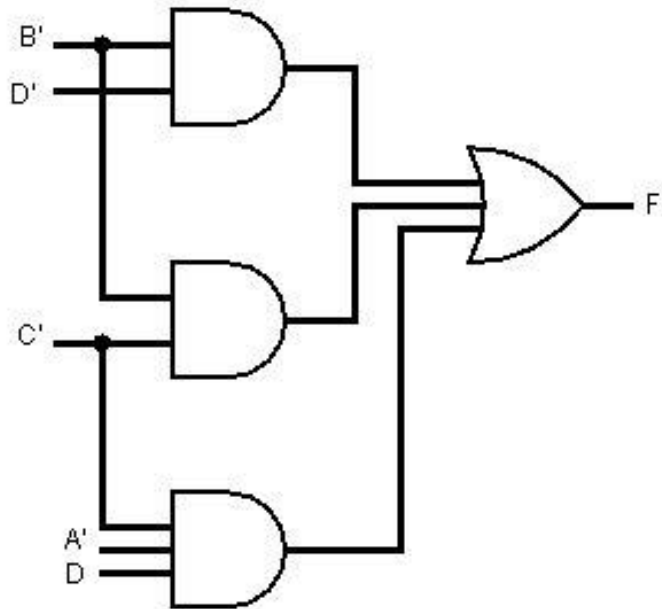


b.  $F = (A' + B')(C' + D')(B' + D)$

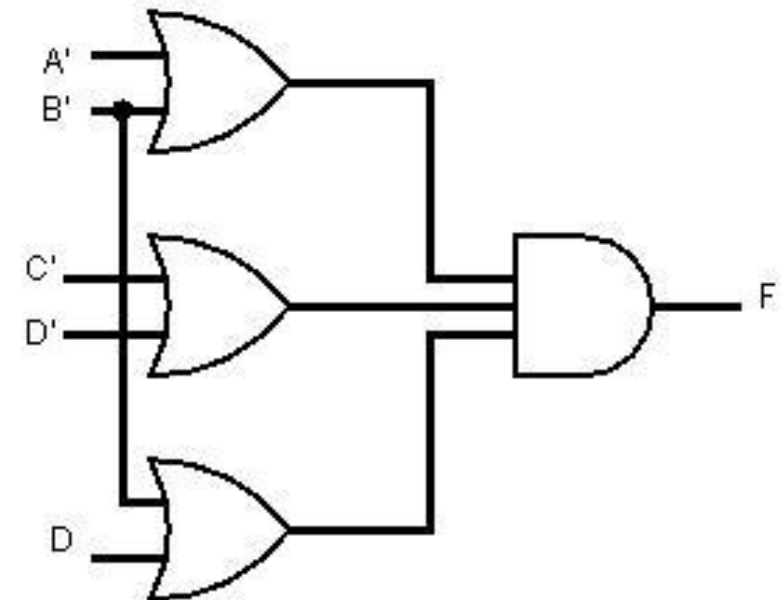
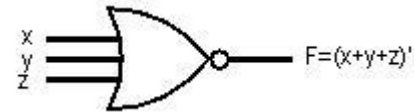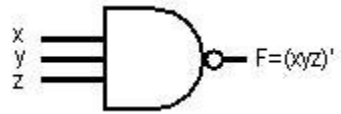
# Last Week..

- Two Level implementations:
  - NOR
  - NAND



# Last Week..

## Rules for NAND and NOR Implementations


	Function to be simplified	Standard form to be used	How to obtain	Implementation	#levels for F
a	F	SOP	Grouping of 1s in map	NAND	2
b	F'	SOP	Grouping of 0s in map	NAND	3
c	F	POS	Complement of F' in (b)	NOR	2
d	F'	POS	Complement of F in (a)	NOR	3

# Other Two Level Implementations

- Gate types: AND, OR, NOR, NAND
- Using one type of gate in the first level and one type of gate in the second level, it is possible to form 16 combinations.
- Among those combinations, ones which have the standard form are as follows:


- AND-OR
- NAND-NAND
- NOR-OR
- OR-AND

OR-AND  
NOR-NOR  
NAND-AND  
AND-NOR

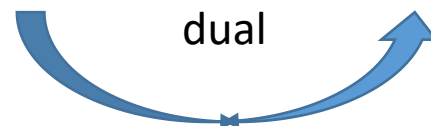

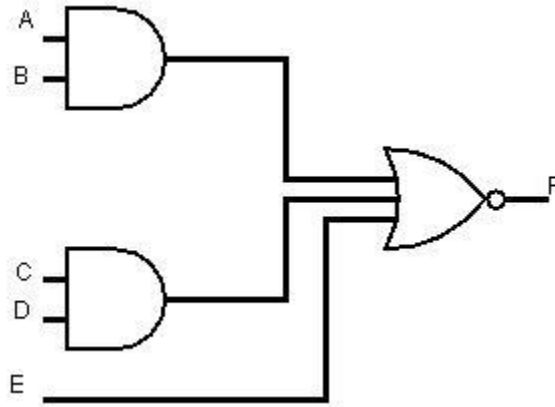
# AND-OR-INVERT Implementation

- AND-NOR, NAND-AND
- $F = (AB + CD + E)'$



AND-NOR

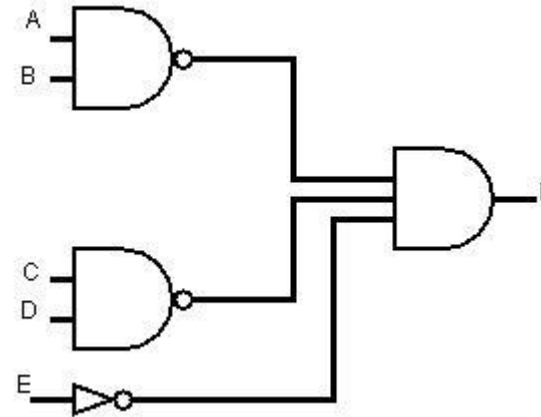


NAND-AND


- Complement of the function can be represented in sum of products form by using 0s in the diagram.
- $F'$  is implemented in AND-OR form (Sum of products)
- $F'$  forms F by the invert operator in the end.
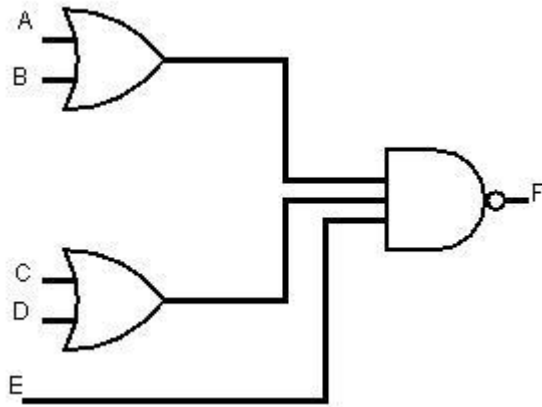
# OR-AND-INVERT Implementation

- OR-NAND and NOR-OR forms both implement OR-AND-INVERT operation.
- $F = [(A+B)(C+D)E]'$



OR-NAND

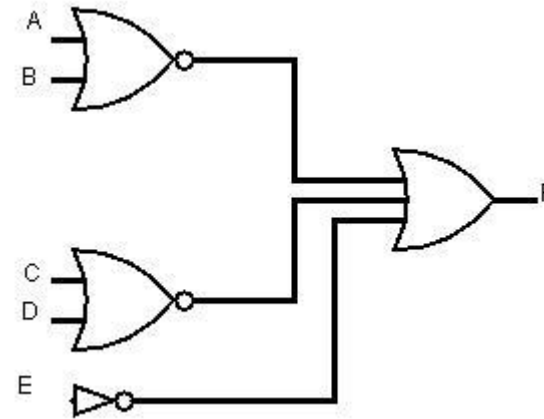

NOR-OR

- OR-AND-INVERT requires a product of sums representation
- Simplify  $F'$  in product of sums form
- Obtain F by inverting  $F'$ .

Equivalent Forms		Implements the function	Simplify $F'$ into	To get an output of
AND-NOR	NAND-AND	AND-OR-INVERT	Sum of products form by combining 0s in the map	F
OR-NAND	NOR-OR	OR-AND-INVERT	Product of sums form by combining 1s in the map and then complementing	F




- Ex:  $F(x,y,z)=\sum(0,6)$  implement the function with the four 2 level forms.


	00	01	11	10
0	1	0	0	0
1	0	0	0	1

- $F' = x'y + xy' + z$
- $F = (x'y + xy' + z)'$

AND-OR-INVERT ?

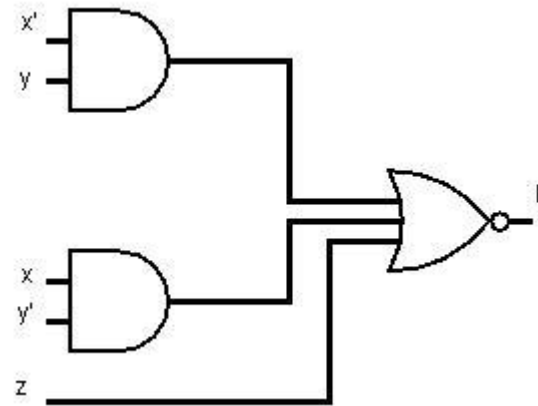

AND-NOR

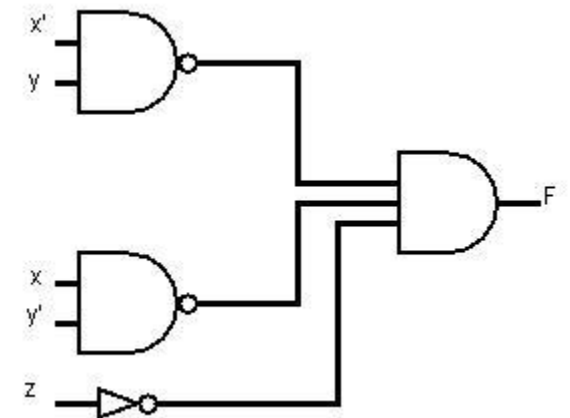


NAND-AND


- Ex:  $F(x,y,z)=\sum(0,6)$

	00	01	11	10
0	1	0	0	0
1	0	0	0	1

OR-AND-INVERT ?

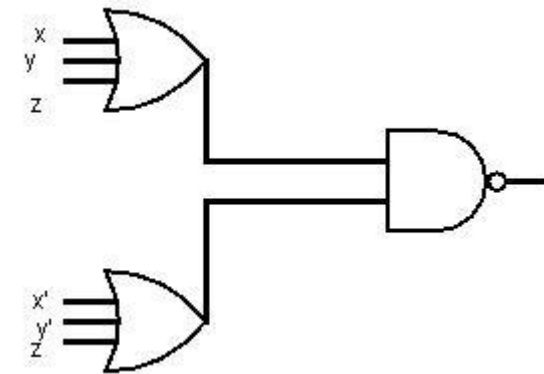

OR-NAND

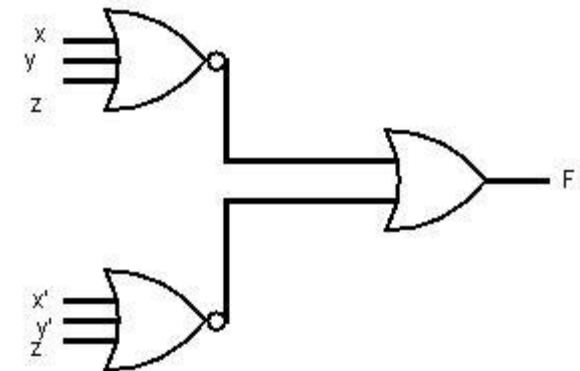

NOR-OR

- $F = x'y'z' + xyz'$  (using 1s in the diagram)
- $F' = [(x+y+z)(x'+y'+z)]'$

# DON'T CARE CONDITIONS

- Upto now, it is assumed that the minterms which are not equal to 1 are equal to 0. In practice, in some applications the function is not specified for certain combinations of variables.
- Ex: Four bit Binary code for the decimal digits has six combinations that are not used and are considered to be unspecified.
- Functions that have unspecified outputs for some input combinations are called incompletely specified functions.
- In most applications, we simply don't care what value is assumed by the function for the unspecified minterms.
- For this reason, those minterms are called don't care conditions.
- These conditions are represented with X's in the diagram. X can take value either 0 or 1.

- Ex. Don't care conditions  $d(w,x,y,z)=\sum(0,2,5)$
- $F(w,x,y,z)=\sum(1,3,7,11,15)$  Simplify the function:

	00	01	11	10
00	X	1	1	X
01		X	1	
11			1	
10			1	

$$F = yz + w'x'$$

$$F = \sum(0,1,2,3,7,11,15)$$

	00	01	11	10
00	X	1	1	X
01		X	1	
11			1	
10			1	

$$F = yz + w'z$$

$$F = \sum(1,3,5,7,11,15)$$

To represent the function in product of sums form:

$$F' = z' + wy'$$

$$F = z(w' + y) = \sum(1,3,5,7,11,15)$$

# Exercise

- Find all prime implicants for the following Boolean function and determine which are essential?
- $F(A,B,C,D)=\sum(0,2,3,5,7,8,10,11,14,15)$

	00	01	11	10
00	1		1	1
01		1	1	
11			1	1
10	1		1	1

- Prime implicants:  $B'D'$ ,  $B'C$ ,  $CD$ ,  $AC$ ,  $A'BD$
- Essential:  $B'D'$ ,  $AC$ ,  $A'BD$
- Non-essential:  $CD$ ,  $B'C$
- $F = B'D' + AC + A'BD + CD$
- $F = B'D' + AC + A'BD + B'C$

# Exercise

- Find all prime implicants for the following Boolean function and determine which are essential?
- $F(A,B,C,D) = \sum(0,2,3,5,7,8,10,11,14,15)$

	00	01	11	10
00	1		1	1
01		1	1	
11			1	1
10	1		1	1

- Essential:  $B'D'$ ,  $AC$ ,  $A'BD$
- Non-essential:  $CD$ ,  $B'C$
- $F = B'D' + AC + A'BD + (CD \text{ or } B'C)$

- Simplify the following Boolean Function, Express the simplified function in sum of minterms form.

- $F(A,B,C,D)=\sum(0,6,8,13,14)$

- $d(A,B,C,D)=\sum(2,4,10)$

- $F=ABC'D+B'D'+CD'$

- $F=\sum(0,2,6,8,10,13,14)$

	00	01	11	10
00	1			X
01	X			1
11		1		1
10	1			X

- Simplify the following Boolean Function, Express the simplified function in sum of minterms form.

- $F(A,B,C,D)=\sum(0,6,8,13,14)$

- $d(A,B,C,D)=\sum(2,4,10)$

- $F=B'D'+BCD'+ABC'D$

- $F=\sum(0,2,6,8,10,13,14)$

	00	01	11	10
00	1			X
01	X			1
11		1		1
10	1			X




- Implement the following Boolean function  $F$ , using two-level forms of logic NAND-AND, AND-NOR, OR-NAND, NOR-OR
- $F(A,B,C,D) = \prod(1,2,3,5,6,7,13,15)$

	00	01	11	10
00	1			
01	1			
11	1			1
10	1	1	1	1

- $F = C'D' + AB' + AD'$

NAND-AND ?

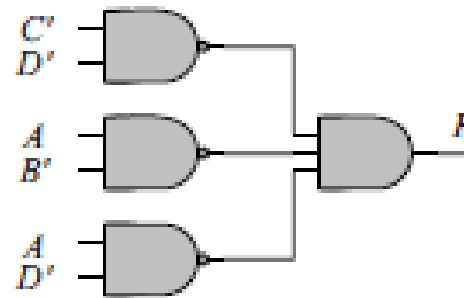


$$F = C'D' + AB' + AD'$$

$$F' = (C'D')'(AB')'(AD')'$$

NAND-AND

AND-NOR

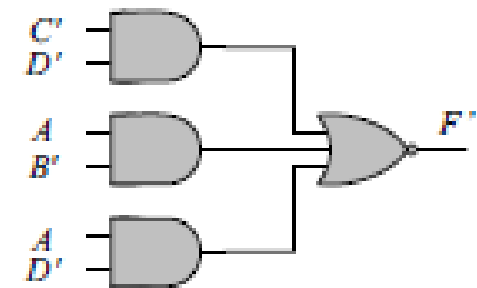


$$F' = [C'D' + AB' + AD']'$$

AND-NOR

- $F = C'D' + AB' + AD'$

	00	01	11	10
00	1			
01	1			
11	1			1
10	1	1	1	1

OR-NAND ?

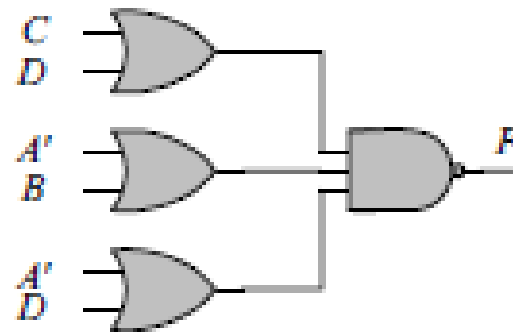


$$F' = (C+D)(A'+B)(A'+D)$$

$$F = [(C+D)(A'+B)(A'+D)]'$$

OR-NAND

NOR-OR ?

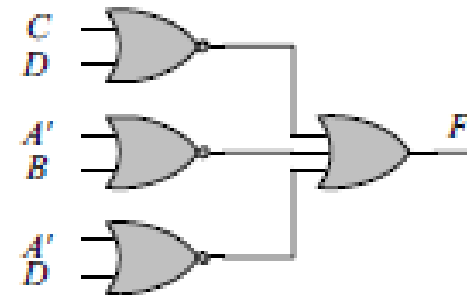

$$F = C'D' + AB' + AD'$$

$$= (C+D)' + (A'+B)' + (A'+D)'$$

NOR-OR