

COM 204 – Digital Logic Systems

Week – 7

Sample Review Problems

Problem 1

- A *PN* flip -flop has four operations; clear to 0, no change, complement, and set to 1, when inputs *P* and *N* are 00, 01, 10 and 11.respectively.
 - Tabulate the characteristic table
 - Derive the characteristic equation
 - Tabulate the excitation table

P	N	Q(t+1)
0	0	0
0	1	Q(t)
1	0	Q'(t)
1	1	1

Problem 1..

- Characteristic table:


P	N	$Q(t+1)$
0	0	0
0	1	$Q(t)$
1	0	$Q'(t)$
1	1	1

- Excitation Table

$Q(t)$	$Q(t+1)$	P	N
0	0	0	x
0	1	1	x
1	0	x	0
1	1	x	1

Characteristic Equation

P	N	$Q(t)$	$Q(t+1)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

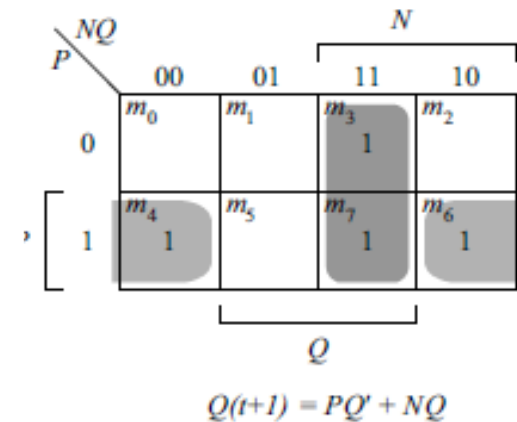


Problem 2

- A sequential circuit with two D flip-flops A and B , two inputs x and y , and one output z is specified by the following next-state and output equations.
 - $A(t+1) = x'y + xB$
 - $B(t+1) = x'A + xB$
 - $z = A$
- Draw the logic diagram of the circuit
- List the state table for the sequential circuit
- Draw the corresponding state diagram

Problem 2..

- $A(t+1) = x'y + xA$
- $B(t+1) = x'B + xA$
- $z = B$

- State Table

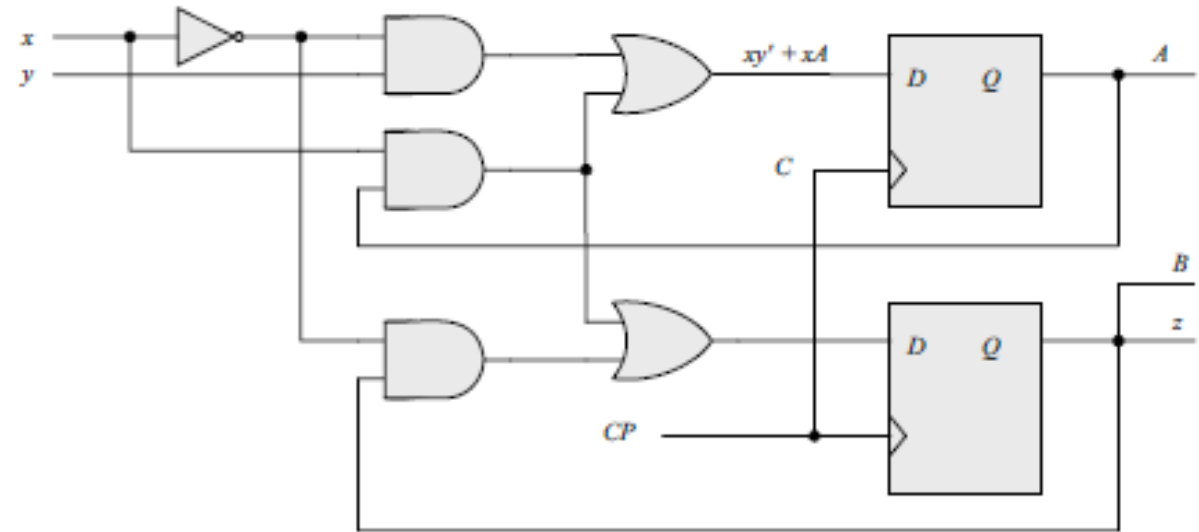


Problem 2.

- $A(t+1) = x'y + xA$
- $B(t+1) = x'B + xA$
- $z = B$

- State Table

Present state		Inputs		Next state		Output
A	B	x	y	A	B	z
0	0	0	0	0	0	0
0	0	0	1	1	0	0
0	0	1	0	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	1	1
0	1	0	1	1	1	1
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	0	0
1	0	0	1	1	0	0
1	0	1	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

State Diagram

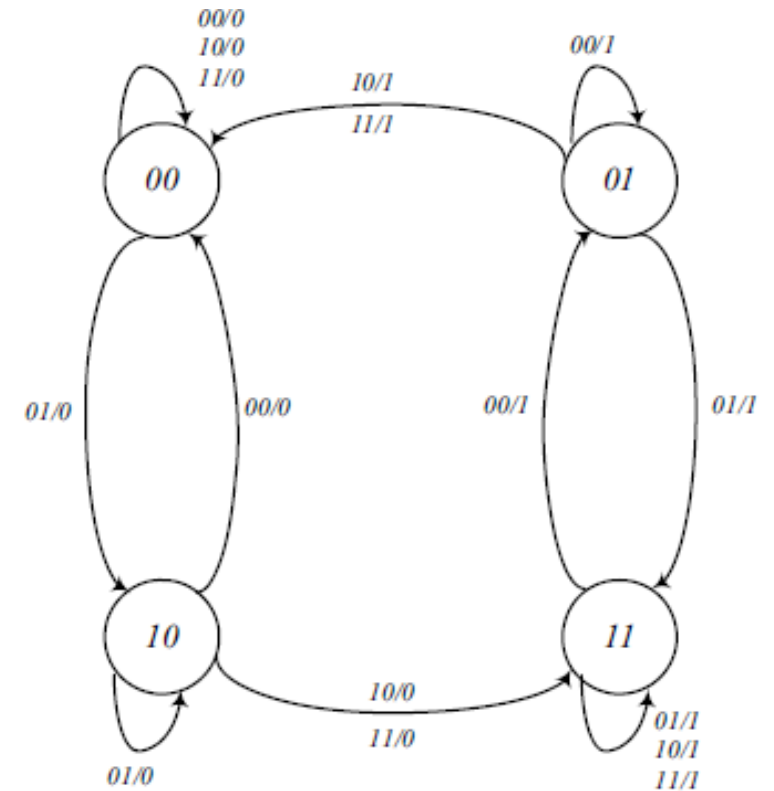


Problem 3

- Derive the state table and the state diagram of the sequential circuit shown in the figure, explain the function that the circuit performs.

- FF input equations:

$$\begin{aligned}T_A &= A + B \\T_B &= A' + B\end{aligned}$$

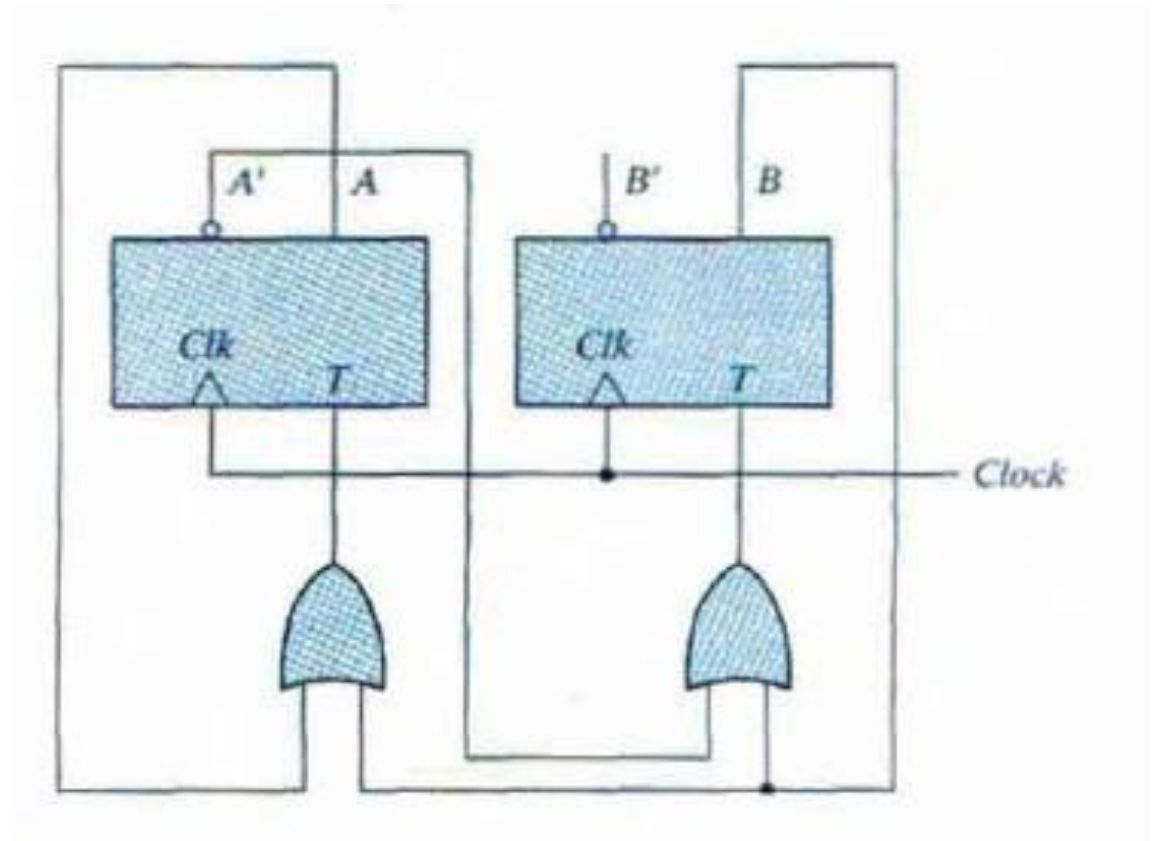

Problem 3..


$$T_A = A + B$$

$$T_B = A' + B$$

- State table:

T	Q(t+1)
0	Q(t)
1	Q'(t)


Present State		Next State		FF-inputs	
A	B	A	B	T_A	T_B
0	0	0	1	0	1
0	1	1	0	1	1
1	0	0	0	1	0
1	1	0	0	1	1

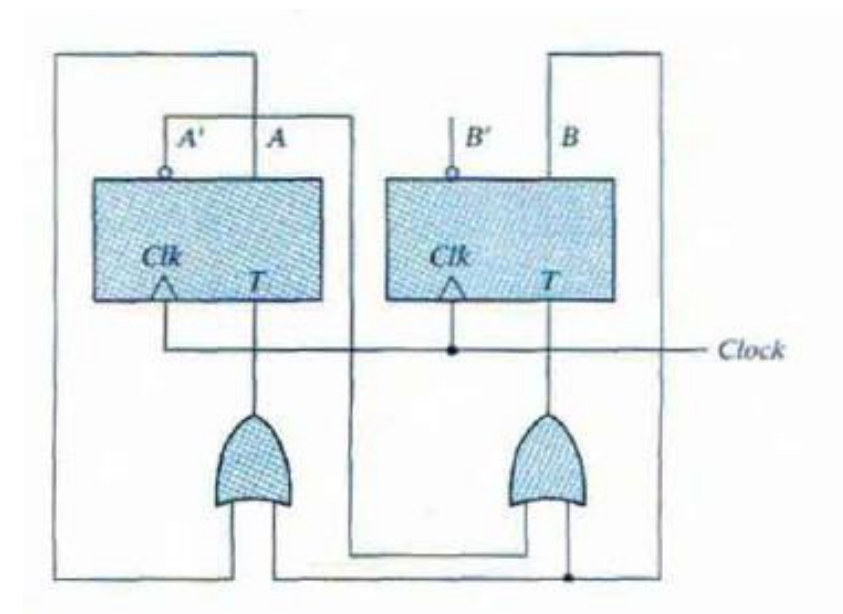

Problem 3..

Present State		Next State		FF-inputs	
A	B	A	B	T _A	T _B
0	0	0	1	0	1
0	1	1	0	1	1
1	0	0	0	1	0
1	1	0	0	1	1

- State diagram:

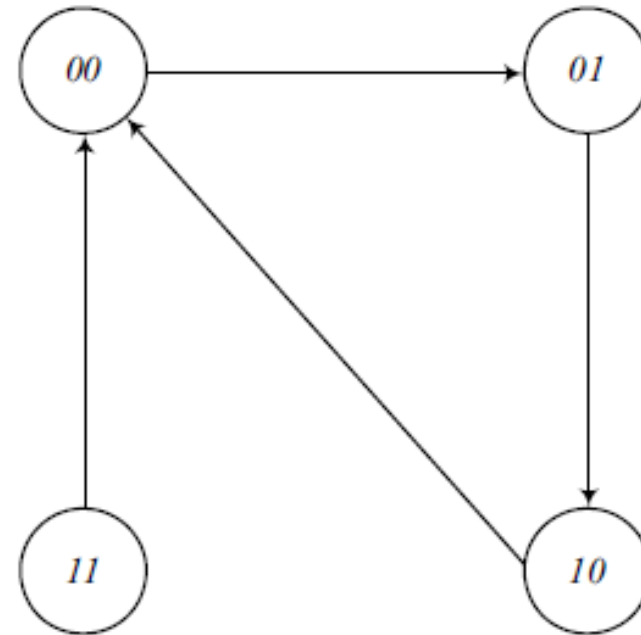


- Explain?


A Counter with a repeated sequence of 00-01-10

Problem 4

- A sequential circuit has three flipflops A, B and C; and one input x_{in} and one output y_{out} . The state diagram is given as follows. The circuit is to be designed by treating unused states as don't care conditions. Analyze the circuit obtained from the design to determine the effect of the unused states.
- A) Use D flip-flops in the design.
- B) Use JK flip-flops in the design.

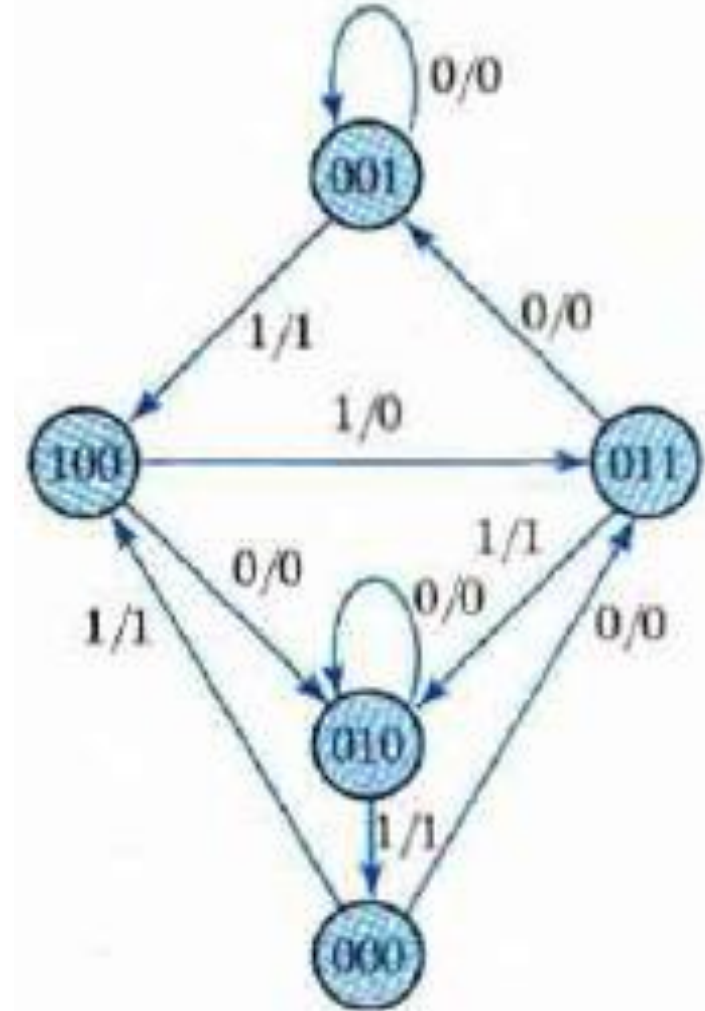

Problem 4..

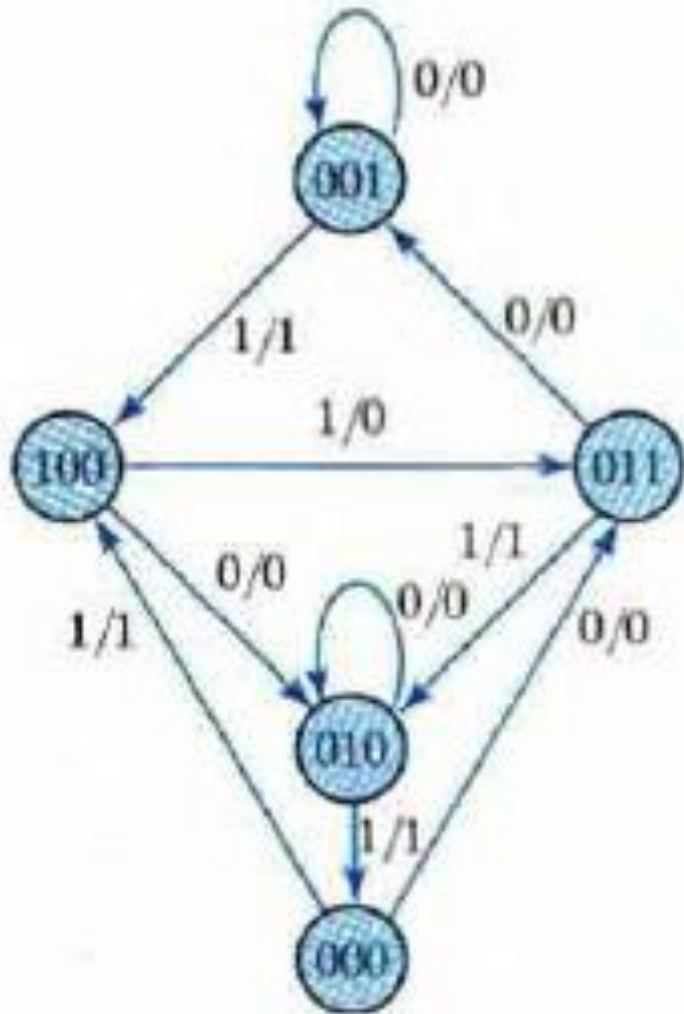

Present State			input	Next State			Output
A	B	C	x	A	B	C	y
0	0	0	0	0	1	1	0
0	0	0	1	1	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	1	0	0	1
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	1	0	1
1	0	0	0	0	1	0	0
1	0	0	1	0	1	1	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Unused states?

101,110,111

Problem 4..

Present state <i>ABC</i>	Input <i>x</i>	Next state <i>ABC</i>	Output <i>y</i>
000	0	011	0
000	1	100	1
001	0	001	0
001	1	100	1
010	0	010	0
010	1	000	1
011	0	001	0
011	1	010	1
100	0	010	0
100	1	011	1

- $d(A,B,C,x) = \sum(?)$
 - 10,11,12,13,14,15

$$D_A = ?$$

$$D_A = A'B'x$$

<i>AB</i> \ <i>Cx</i>		<i>C</i>			
		00	01	11	10
<i>A</i>	00	m_0	m_1 1	m_3 1	m_2
	01	m_4	m_5	m_7	m_6
	11	m_{12} x	m_{13} x	m_{15} x	m_{14} x
	10	m_8	m_9	m_{11} x	m_{10} x

<i>AB</i> \ <i>Cx</i>		<i>C</i>			
		00	01	11	10
<i>A</i>	00	m_0 1	m_1	m_3	m_2 1
	01	m_4	m_5	m_7	m_6 1
	11	m_{12} x	m_{13} x	m_{15} x	m_{14} x
	10	m_8	m_9 1	m_{11} x	m_{10} x

$$D_C = Cx' + Ax + A'B'x'$$

$$D_B = ?$$

$$D_B = A + C'x' + BCx$$

<i>AB</i> \ <i>Cx</i>		<i>C</i>			
		00	01	11	10
<i>A</i>	00	m_0 1	m_1	m_3	m_2
	01	m_4 1	m_5	m_7 1	m_6
	11	m_{12} x	m_{13} x	m_{15} x	m_{14} x
	10	m_8 1	m_9 1	m_{11} x	m_{10} x

<i>AB</i> \ <i>Cx</i>		<i>C</i>			
		00	01	11	10
<i>A</i>	00	m_0	m_1 1	m_3 1	m_2
	01	m_4	m_5 1	m_7 1	m_6
	11	m_{12} x	m_{13} x	m_{15} x	m_{14} x
	10	m_8	m_9	m_{11} x	m_{10} x

$$y = A'x$$

Problem 4..

- What happens at unused states?


- 101?
 - $\rightarrow 011$
- 110?
 - $x=0 \rightarrow 010$
 - $x=1 \rightarrow 011$
- 111?
 - $\rightarrow 011$

$$D_A = A'B'x$$

$$D_B = A + C'x' + BCx$$

$$D_C = Cx' + Ax + A'B'x'$$

The machine is self-correcting, i.e., the unused states transition to known states.

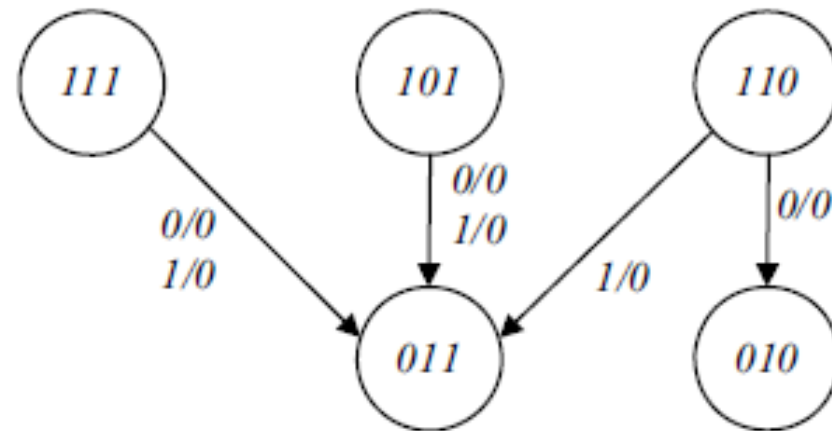

Problem 4..

- With JK Flipflops

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Present State			input	Next State			Output	FF inputs					
A	B	C	x	A	B	C	y	JA	KA	JB	KB	JC	KC
0	0	0	0	0	1	1	0	0	X				
0	0	0	1	1	0	0	1	1	X				
0	0	1	0	0	0	1	0	0	X				
0	0	1	1	1	0	0	1						
0	1	0	0	0	1	0	0						
0	1	0	1	0	0	0	1						
0	1	1	0	0	0	1	0						
0	1	1	1	0	1	0	1						
1	0	0	0	0	1	0	0						
1	0	0	1	0	1	1	0						
1	0	1	0	X	X	X		X	X	X	X	X	X
1	0	1	1	X	X	X		X	X	X	X	X	X
1	1	0	0	X	X	X		X	X	X	X	X	X
1	1	0	1	X	X	X		X	X	X	X	X	X
1	1	1	0	X	X	X		X	X	X	X	X	X

Problem 4..

- State table is the same

<i>Flip-flop inputs</i>					
J_A	K_A	J_B	K_B	J_C	K_C
0	x	1	x	1	x
1	x	0	x	0	x
0	x	0	x	x	0
1	x	0	x	x	1
0	x	x	0	0	x
0	x	x	1	0	x
0	x	x	1	x	0
0	x	x	0	x	1
x	1	1	x	0	x
x	1	1	x	1	x

$$\begin{aligned}
 J_A &= B'x & K_A &= 1 \\
 J_B &= A + C'x' & K_B &= C'x + Cx' \\
 J_C &= Ax + A'B'x' & K_C &= x \\
 y &= A'x
 \end{aligned}$$

The machine is self-correcting
because $K_A = 1$.

$$101 \rightarrow 0_ \quad \begin{matrix} J_A = \\ K_A = 1 \end{matrix}$$

$$110 \rightarrow 0_$$

$$111 \rightarrow 0_$$

Good Luck in the exams.